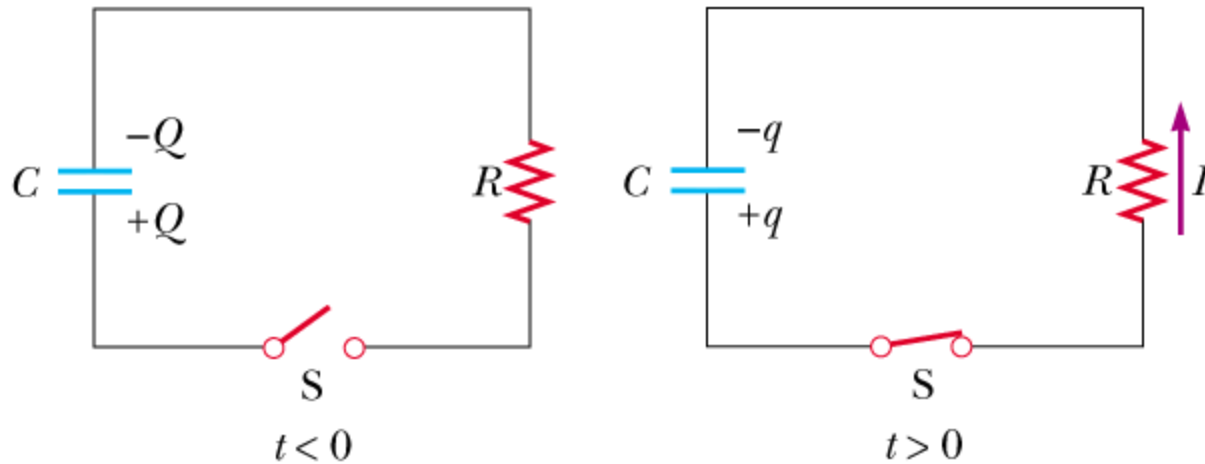


Announcements

1. Vote on time for extra review session for Friday afternoon (2/7/03) – 2PM
3PM
2. Today's topics –
Continue discussion of RC circuits
General strategies for analyzing DC circuits
3. Friday – review for first hour exam on Monday

RC circuit -- Discharging a capacitor through a resistor



initial condition:

$$q(t=0) = Q$$

after the switch is closed:

$$-\frac{q}{C} - IR = 0$$

$$\Rightarrow -\frac{q}{C} - \frac{dq}{dt} R = 0$$


Analysis:

$$\begin{aligned} -\frac{q}{C} - \frac{dq}{dt} R &= 0 \\ \frac{dq}{dt} &= -\frac{1}{RC} q \\ \frac{dq}{q} &= -\frac{1}{RC} dt \\ \ln\left(\frac{q(t)}{Q}\right) &= -\frac{t}{RC} \end{aligned}$$

Result :

$$q(t) = Q \left(e^{-t/(RC)} \right)$$
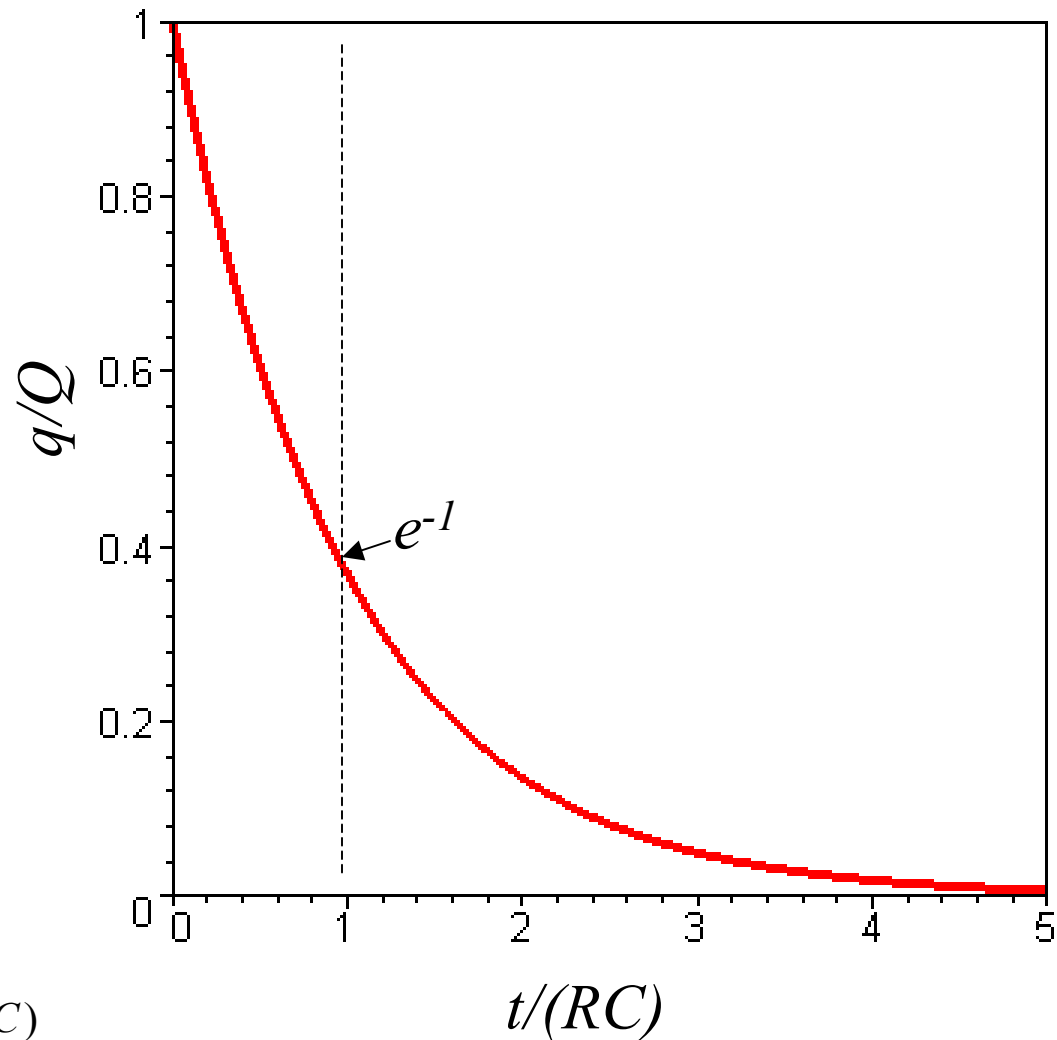
$$I(t) \equiv \frac{dq}{dt} = -\frac{Q}{RC} e^{-t/(RC)}$$



General method for solving first-order linear differential equation

Assume we want to find $q(t)$ in terms of constants A, B, C .

$$A \frac{dq}{dt} + Bq + C = 0$$

Try solution form: $q(t) = Xe^{Yt} + Z$

Substitute into equation: $AX(Y)e^{Yt} + B(Xe^{Yt} + Z) + C = 0$

This must be true for all times t .

$$BZ + C = 0 \quad \Rightarrow Z = -C / B$$


$$AXY + BX = 0 \quad \Rightarrow Y = -B / A$$

X determined from initial conditions

$$\text{If } q(t=0) = Q \quad \Rightarrow X = Q + C / B$$

$$q(t) = Qe^{-Bt/A} + \frac{C}{B}(e^{-Bt/A} - 1)$$

Example circuit:

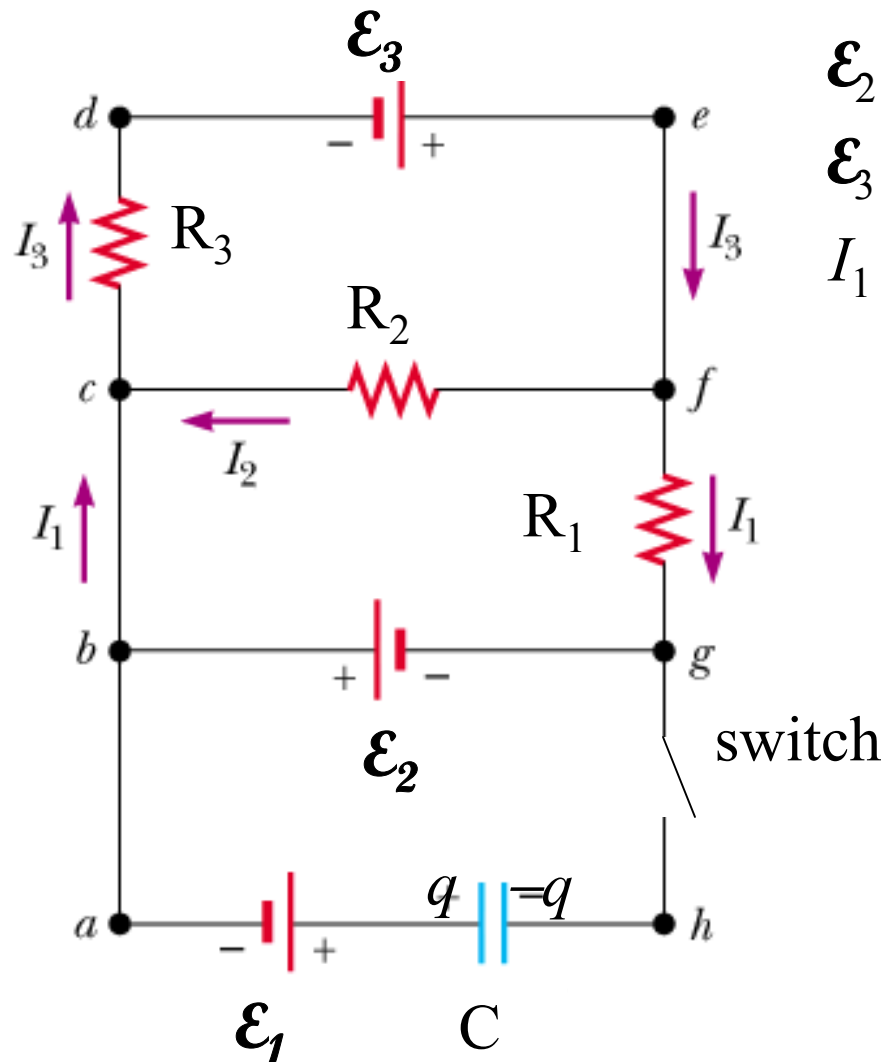

Analysis with switch open :

$$\mathcal{E}_2 + I_2 R_2 - I_1 R_1 = 0$$

$$\mathcal{E}_3 - I_2 R_2 - I_3 R_3 = 0$$

$$I_1 + I_2 = I_3$$

$$-I_1 R_1 + I_2 R_2 = -\mathcal{E}_2$$

$$-I_2 R_2 - I_3 R_3 = -\mathcal{E}_3$$

$$I_1 + I_2 - I_3 = 0$$

$$R_1 = R_3 = 5\Omega, R_2 = 3\Omega$$

$$\mathcal{E}_1 = 3V, \mathcal{E}_2 = 8V, \mathcal{E}_3 = 4V$$

$$C = 6 \times 10^{-6} F$$

Solution strategy:

$$-I_1 R_1 + I_2 R_2 = -\mathcal{E}_2$$

$$-I_2 R_2 - I_3 R_3 = -\mathcal{E}_3$$

$$I_1 + I_2 - I_3 = 0$$

$$aX + bY + cZ = A$$

$$dX + eY + fZ = B$$

$$gX + hY + iZ = C$$


→

$$a'X = A'$$

$$d'X + e'Y = B'$$

$$gX + hY + iZ = C$$

Example circuit:

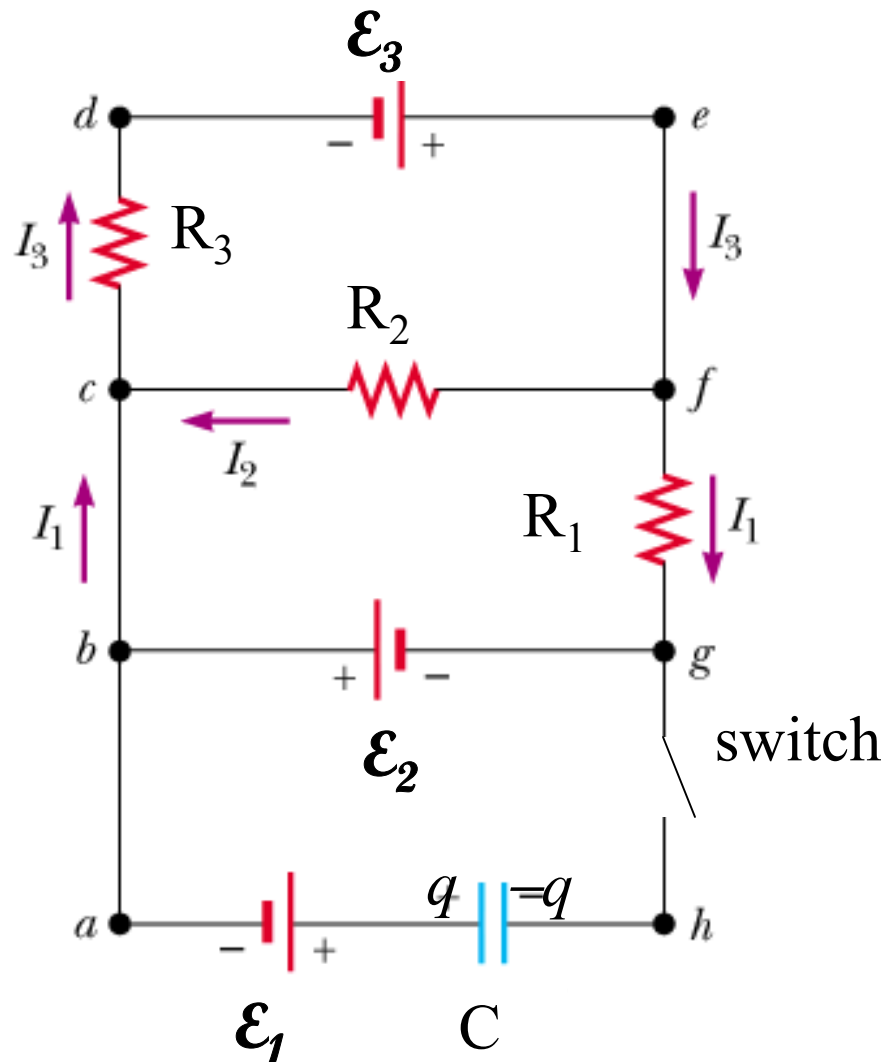

$$R_1 = R_3 = 5\Omega, R_2 = 3\Omega$$

$$\mathcal{E}_1 = 2V, \mathcal{E}_2 = 8V, \mathcal{E}_3 = 4V$$

$$C = 6 \times 10^{-6} F$$


Result with open switch:

$$I_1 = 1.381818 \text{ A}$$

$$I_2 = -0.363636 \text{ A}$$

$$I_3 = 1.018182 \text{ A}$$

Example circuit:

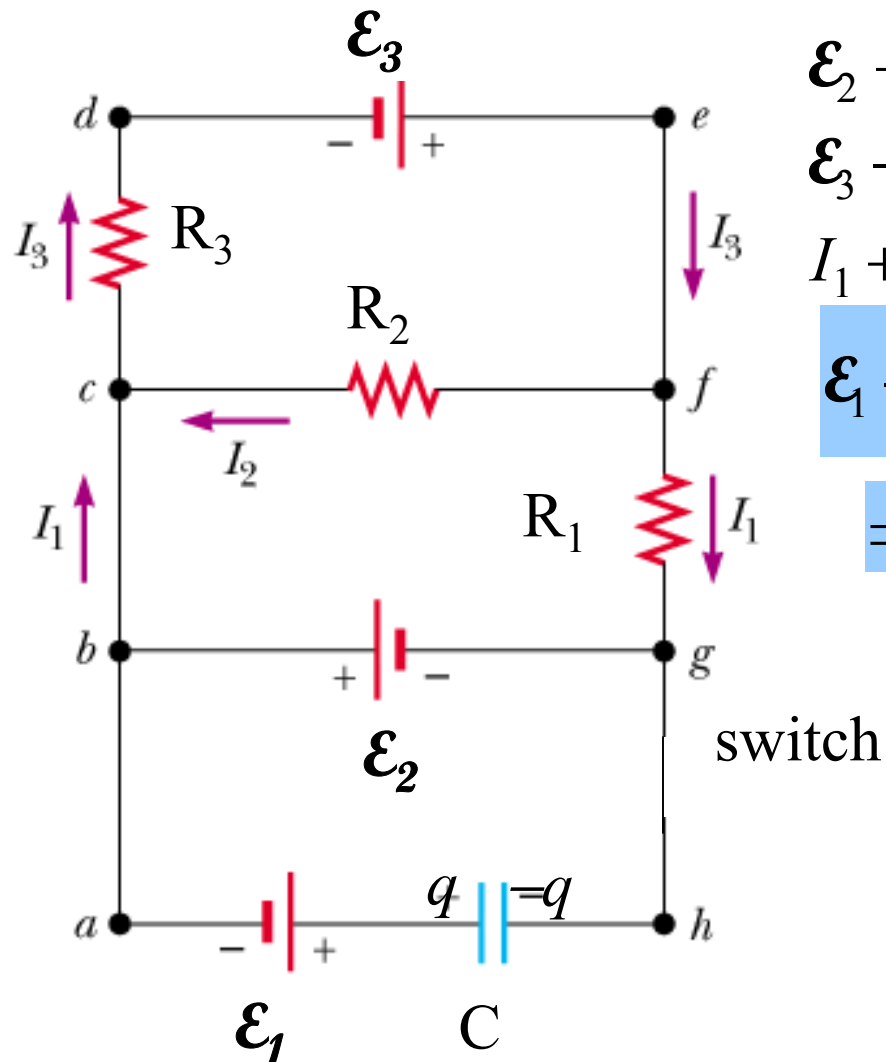

Analysis with switch closed :

$$\mathcal{E}_2 + I_2 R_2 - I_1 R_1 = 0$$

$$\mathcal{E}_3 - I_2 R_2 - I_3 R_3 = 0$$

$$I_1 + I_2 = I_3$$

$$\mathcal{E}_1 - \frac{q}{C} + \mathcal{E}_2 = 0$$

$$\Rightarrow q = (\mathcal{E}_1 + \mathcal{E}_2)C = 6.6 \times 10^{-5} C$$

$$R_1 = R_3 = 5\Omega, R_2 = 3\Omega$$

$$\mathcal{E}_1 = 3V, \mathcal{E}_2 = 8V, \mathcal{E}_3 = 4V$$

$$C = 6 \times 10^{-6} F$$

Shortcuts – using equivalent circuits


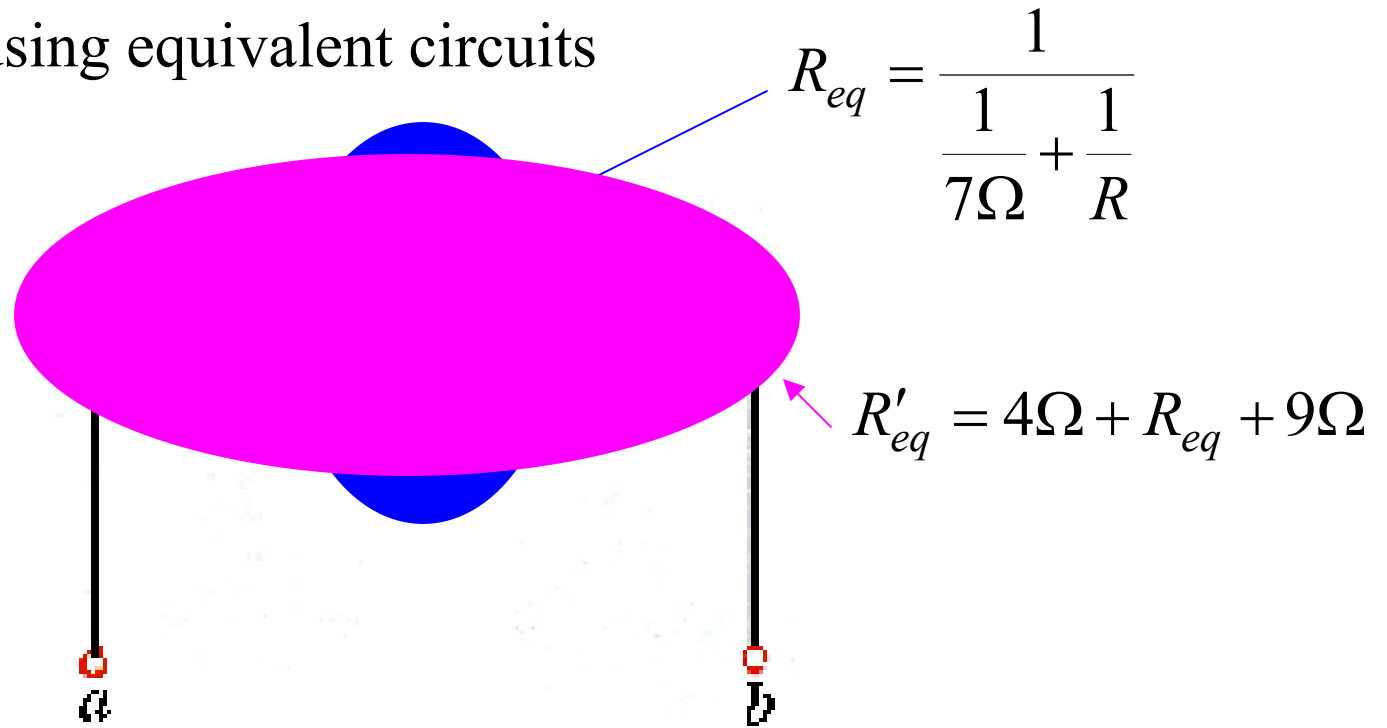
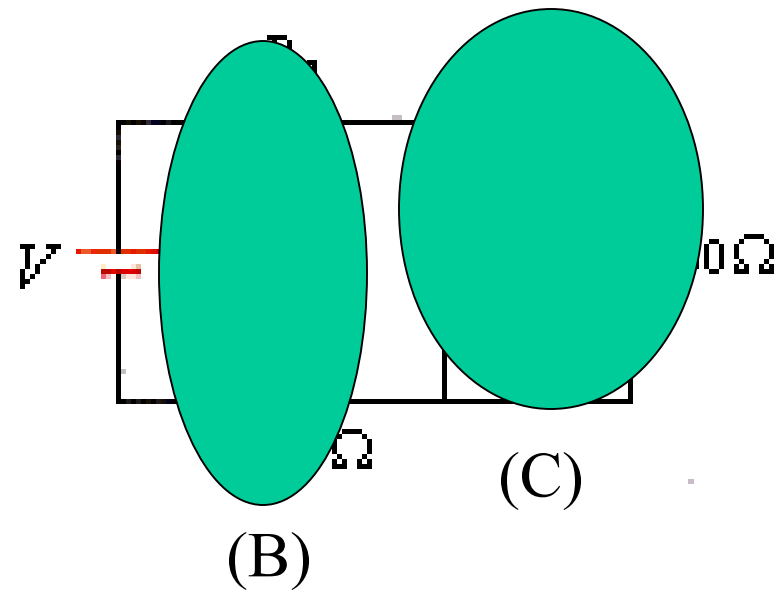


Figure P28.6.

Peer instruction question:


Which of these are NOT in parallel?

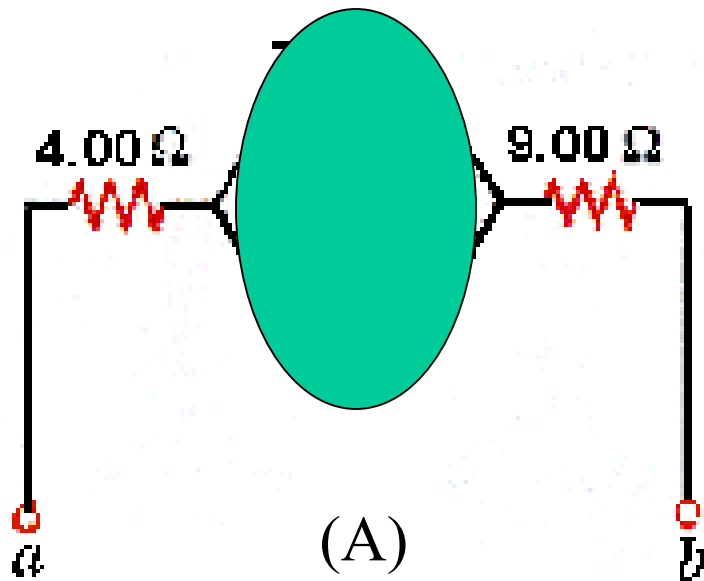

(C)

Peer instruction question:

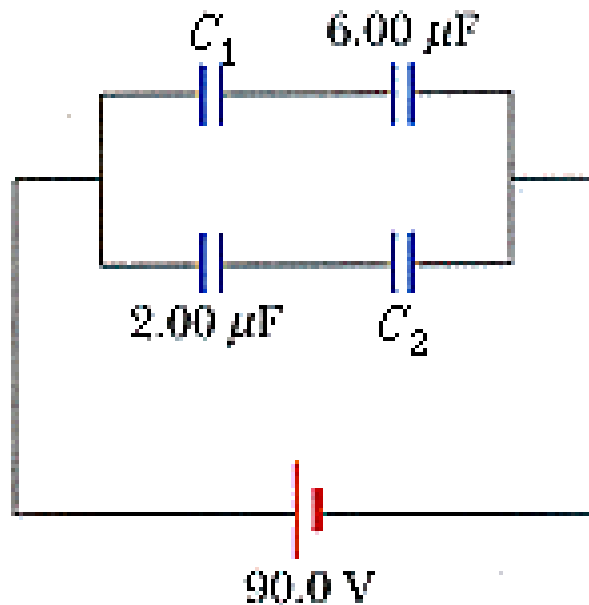Which of these capacitors are in parallel?



(A) C_1 & $6\mu\text{F}$

(B) C_1 & $2\mu\text{F}$

(C) $C_1 + 6\mu\text{F}$ & $C_2 + 2\mu\text{F}$

(D) None these answers

Homework examples:

1. [SB5 28.P.18. (47538)] The ammeter shown in Figure P28.18 reads 2.20 A. Find I_1 , I_2 , and ϵ .

$I_1 =$ $\times [0.571] \text{ A}$

$I_2 =$ ✗ [1.63] A

$\epsilon =$ $\times [14.3] \text{ V}$

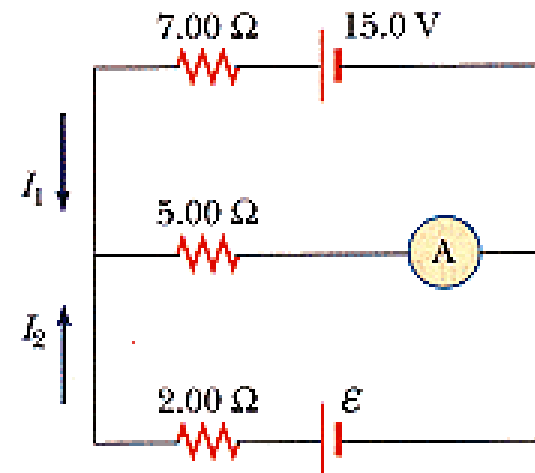


Figure P28.18.