

Announcements

1. First hour exam – Friday, February 4, 2004 – covering Chapters 22-28.

May bring 1 8½” x 11” sheet of paper to the exam (to be turned in with your exam papers).

The exam will be proctored by Professor G. Holzwarth.

Practice exam available on website.

Review sessions: Tuesday 2/1/05 at 6-7 PM

Wednesday 2/2/05 (class time)

2. Today’s topic

Current, power, circuits

1. [HRW6 27.P.007.] A fuse in an electric circuit is a wire that is designed to melt, and thereby open the circuit, if the current exceeds a predetermined value. Suppose that the material to be used in a fuse melts when the current density rises to 410 A/cm^2 . What diameter of cylindrical wire should be used to limit the current to 0.65 A ?

 m

4. [HRW6 27.P.026.] In Earth's lower atmosphere there are negative and positive ions, created by radioactive elements in the soil and cosmic rays from space. In a certain region, the atmospheric electric field strength is **110** V/m, directed vertically down. This field causes singly charged positive ions, **690** per cm^3 , to drift downward and singly charged negative ions, **580** per cm^3 , to drift upward (Fig. 27-24). The measured conductivity is $2.70 \times 10^{-14} \text{ } \Omega \cdot \text{m}$.

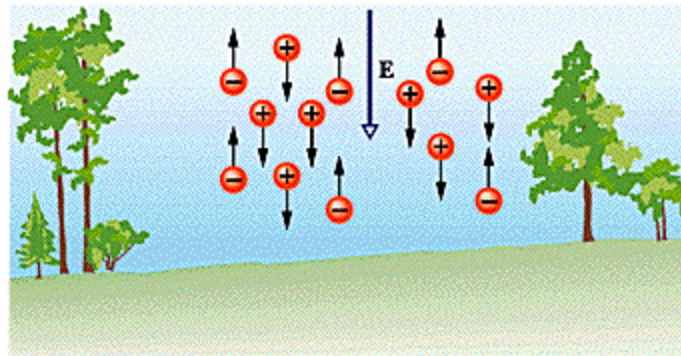


Figure 27-24.

Calculate

(a) the ion drift speed, assumed to be the same for positive and negative ions, and

cm/s

(b) the current density.

A/m^2

Electrical current in a wire

Approximately follows Ohm's law: $\Delta V = IR$

The resistance R depends on properties of the materials

$$R = \frac{m\Delta L}{q^2 n \tau A} \equiv \rho \frac{\Delta L}{A}$$

$$-E = \Delta V / \Delta L$$


The diagram shows a cylindrical wire segment of length ΔL and cross-sectional area A . Inside the wire, several jagged arrows represent the random motion of electrons. A horizontal arrow above the wire points to the left, labeled $-E = \Delta V / \Delta L$, indicating the direction of the electric field.

m electron mass

q electron charge

n number of electrons/volume

τ time between collisions

In general R depends on temperature T .

Electrical power associated with current in a wire

$$dU = dq\Delta V$$

$$\Rightarrow \underbrace{\frac{dU}{dt}} = \frac{dq}{dt} \Delta V \equiv I\Delta V$$

\mathcal{P} (electrical power)

unit: 1 J/s = 1 Watt

$$\mathcal{P} = I\Delta V = I^2 R = \frac{(\Delta V)^2}{R}$$

➔ \mathcal{P} represents rate of energy transfer while current passes through wire

Consider a 60 W light bulb, connected to a 120 V voltage source.



What is the current passing through the wire in the bulb?

- (A) 0.5 A (B) 1.0 A (C) 30 A (D) 240 A

What is the resistance of the wire in the bulb?


- (A) 0.5 Ω (B) 1.0 Ω (C) 30 Ω (D) 240 Ω

Online Quiz for Lecture 7
Electrical current -- Jan. 28, 2005

Suppose that you connect a light bulb (either 30-W or 60-W) to a 120 V voltage source.

1. What is the resistance (in Ω) in the 30-W bulb?
(a) 0.25 (b) 4 (c) 480 (d) 3600
2. What is the current (in Amps) in the 30-W bulb?
(a) 0.25 (b) 4 (c) 480 (d) 3600
3. What is the resistance (in Ω) in the 60-W bulb?
(a) 0.5 (b) 2 (c) 240 (d) 7200
4. What is the current (in Amps) in the 60-W bulb?
(a) 0.5 (b) 2 (c) 240 (d) 7200

Connecting resistors in series:

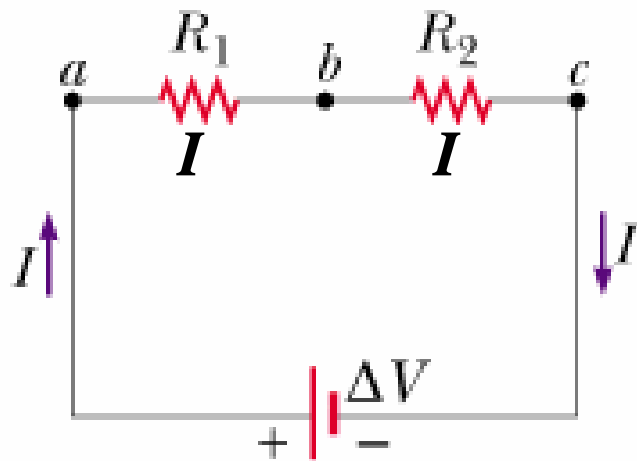


The same current I passes through both resistors R_1 and R_2 .

$$\begin{aligned}\Delta V &= I R_1 + I R_2 \\ &= I (R_1 + R_2)\end{aligned}$$

➔ For resistors connected in series:

$$R_{eq} = \sum_i R_i$$

Resistors connect in parallel

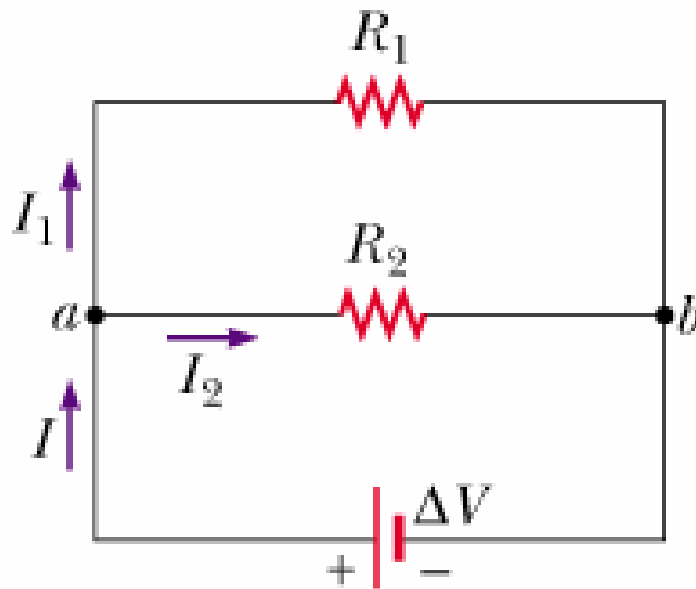

The same voltage ΔV passes through each resistor:

$$\Delta V = I_1 R_1 = I_2 R_2$$


$$I = I_1 + I_2$$

$$\Delta V = I R_{eq}$$

➔ For resistors connected in parallel:

$$\frac{1}{R_{eq}} = \sum_i \frac{1}{R_i}$$

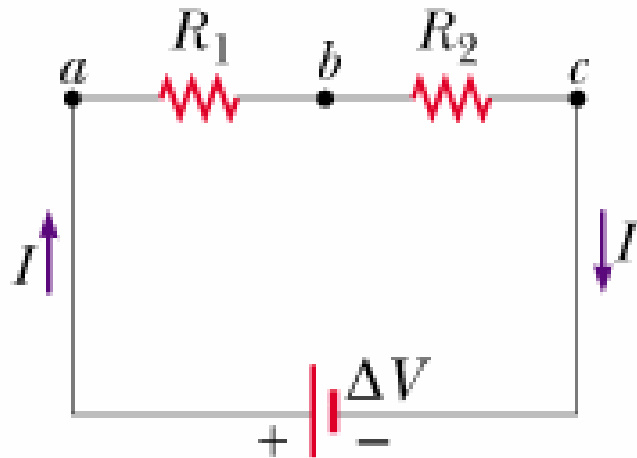Example: $\Delta V = 100 \text{ V}$ $R_1 = 2 \Omega$ $R_2 = 3 \Omega$




$$R_{eq} = R_1 + R_2 = 2\Omega + 3\Omega = 5\Omega$$

$$I = \frac{\Delta V}{R_{eq}} = \frac{100V}{5\Omega} = 20A$$

$$V_1 = IR_1 = 40V \quad V_2 = IR_2 = 60V$$
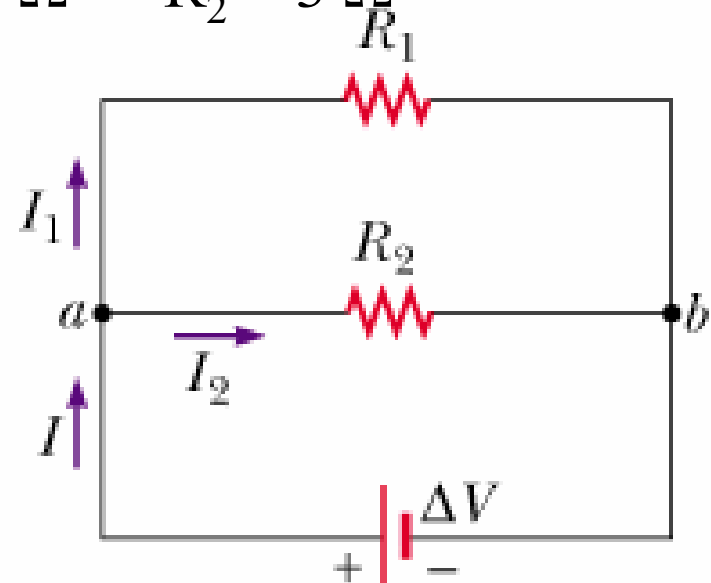
$$\mathcal{P} = I_1 V_1 + I_2 V_2 = 2000W$$




$$V_1 = I_1 R_1 = I_2 R_2 = V$$

$$I_1 = \frac{V}{R_1} = \frac{100V}{2\Omega} = 50A$$

$$I_2 = \frac{V}{R_2} = \frac{100V}{3\Omega} = 33.333A$$
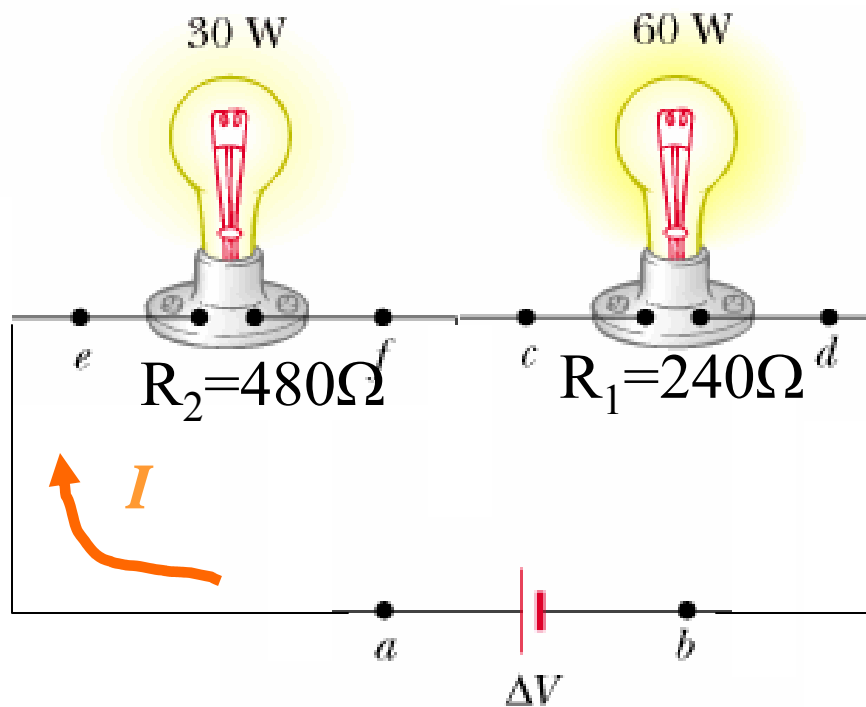
$$\mathcal{P} = I_1 V_1 + I_2 V_2 = 8333.33333W$$



$$\Delta V = I (R_1 + R_2)$$

$$I = 0.167 \text{ A}$$

$$\mathcal{P}_2 = 13.33 \text{ W}$$

$$\mathcal{P}_1 = 6.67 \text{ W}$$

Consider the circuit shown on the left.
 How much current is running in each light bulb when $\Delta V = 120 \text{ V}$? (Note: the power rating of each bulb is valid only when they are connected to a 120 V voltage source.)


$$I_2 = \frac{\mathcal{P}_2}{\Delta V} = 0.25 \text{ A}$$

$$R_2 = \frac{(\Delta V)^2}{\mathcal{P}_2} = 480 \Omega$$

$$I_1 = \frac{\mathcal{P}_1}{\Delta V} = 0.5 \text{ A}$$

$$R_1 = \frac{(\Delta V)^2}{\mathcal{P}_1} = 240 \Omega$$

$$I = I_1 + I_2 = 0.75 \text{ A}$$

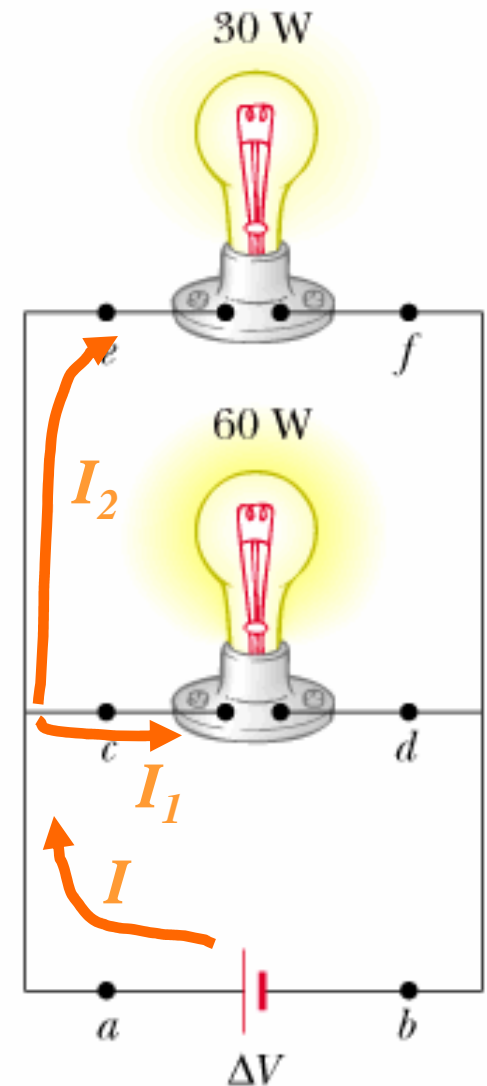

Peer instruction question

Suppose you connect two devices, each with a resistance of $100\ \Omega$ in *parallel* to a $120\ \text{V}$ voltage source. What is the total current in the circuit?

(A) $0.6\ \text{A}$ (B) $1.2\ \text{A}$ (C) $2.4\ \text{A}$ (D) $4.8\ \text{A}$

Suppose you connect two devices, each with a resistance of $100\ \Omega$ in *series* to a $120\ \text{V}$ voltage source. What is the total current in the circuit?



(A) $0.6\ \text{A}$ (B) $1.2\ \text{A}$ (C) $2.4\ \text{A}$ (D) $4.8\ \text{A}$

Voltage sources

- Batteries (chemical reactions)
- Solar cells (conversion of solar energy to voltage output)
- Generators (conversion of mechanical energy to voltage output)

General terminology – “electromotive force” – emf, \mathcal{E}

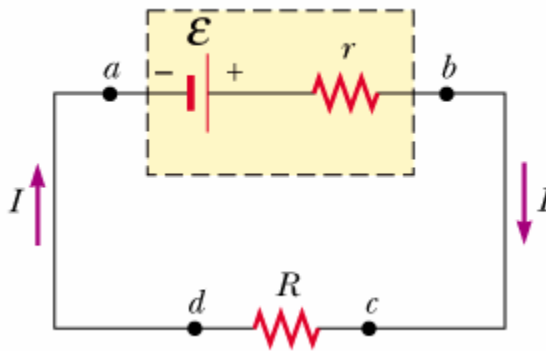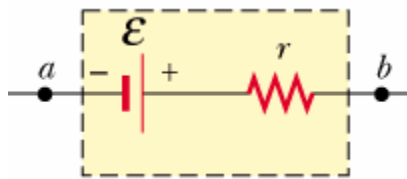Real emf's often have energy losses during operation so that the ideal voltage \mathcal{E} is reduced. This energy loss can be modeled by an internal resistance r represented by the equivalent circuit:




In this case the current is then determined by

$$\mathcal{E} = (r + R)I$$

$$I = \frac{\mathcal{E}}{r + R}$$

Analysis of DC circuits:

Elements:

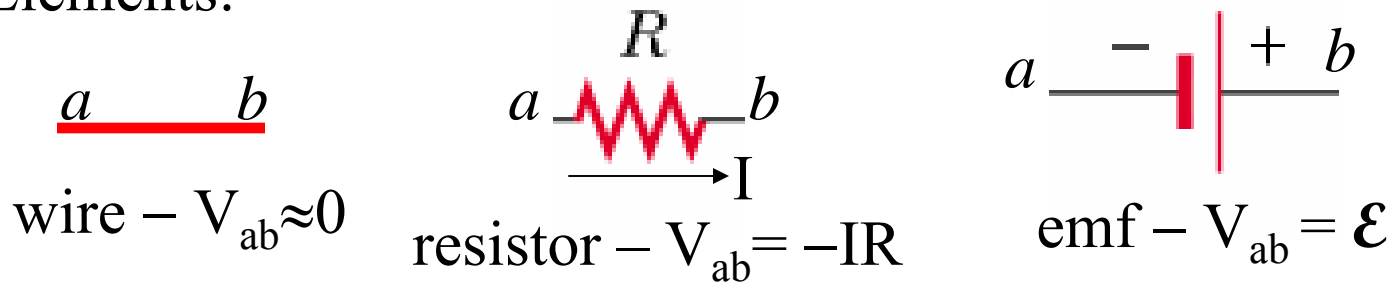


The principles:

Kirchhoff's rules

At any wire function: $\sum I_{in} = \sum I_{out}$

For any closed wire loop: $\sum \Delta V = 0$


Example:

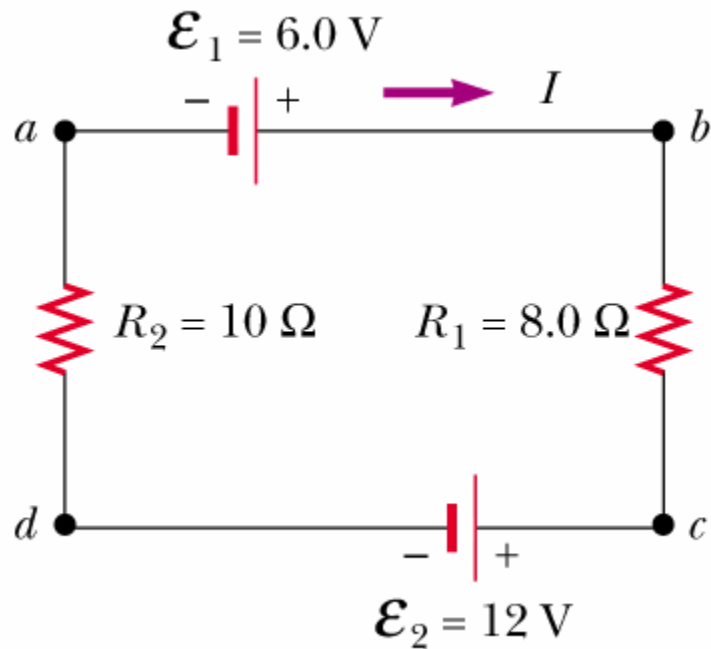

$$\mathcal{E}_1 - IR_1 + (-\mathcal{E}_2) - IR_2 = 0$$

$$I = \frac{\mathcal{E}_1 - \mathcal{E}_2}{R_1 + R_2} = -0.33 \text{ A}$$

Example:

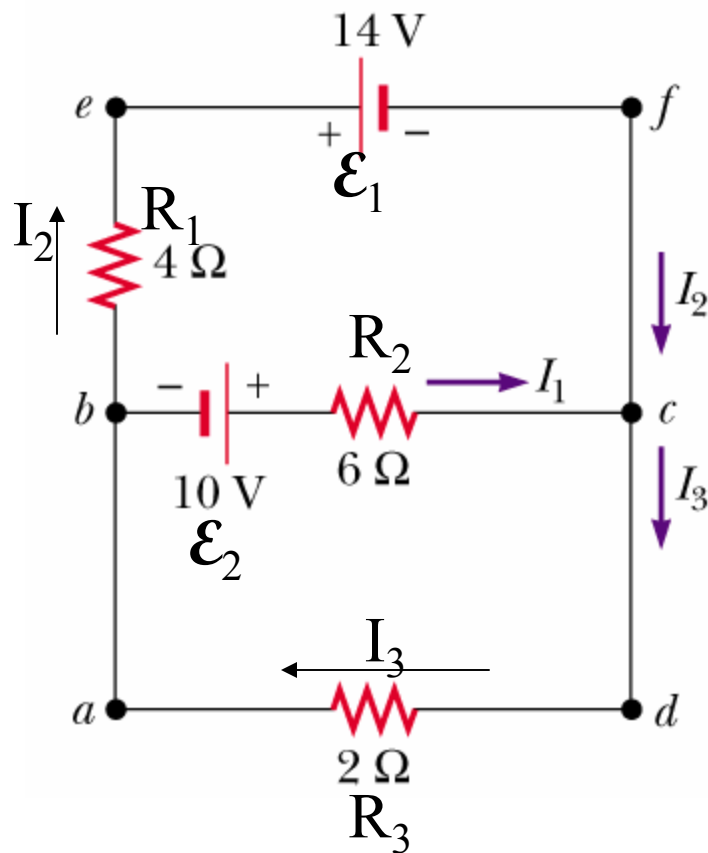

$$-\mathcal{E}_1 + I_1 R_2 - \mathcal{E}_2 - I_2 R_1 = 0$$

$$\mathcal{E}_2 - I_1 R_2 - I_3 R_3 = 0$$

$$I_1 + I_2 = I_3$$

$$I_1 = 2\text{ A}$$

$$I_2 = -3\text{ A}$$

$$I_3 = -1\text{ A}$$