


## Announcements

1. Hour exam results – hopefully available Wed.
  - Will go over exam at Tuesday's tutorial ( 6 PM)
    - Time change????
    - Fresh start on homework
2. Today's topic – RC circuits
  - Kirchhoff's analysis
  - Differential equations
  - Time dependent currents and charges

## Analysis of DC circuits:


### Elements:

wire

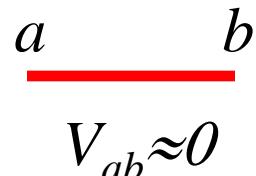


$$V_{ab} \approx 0$$

resistor

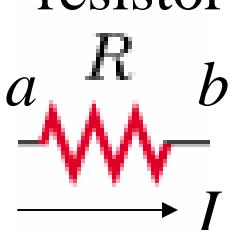


$$V_{ab} = -IR$$

capacitor

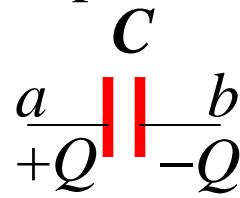

$$V_{ab} = -Q/C$$

emf

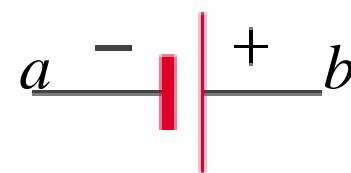


$$V_{ab} = \mathcal{E}$$

The principles:

Kirchhoff's rules

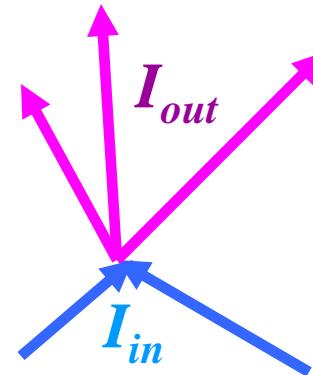
$$\text{At any wire junction: } \sum I_{in} = \sum I_{out}$$



$$\text{For any closed wire loop: } \sum \Delta V = 0$$




Circuit with an emf and resistor:

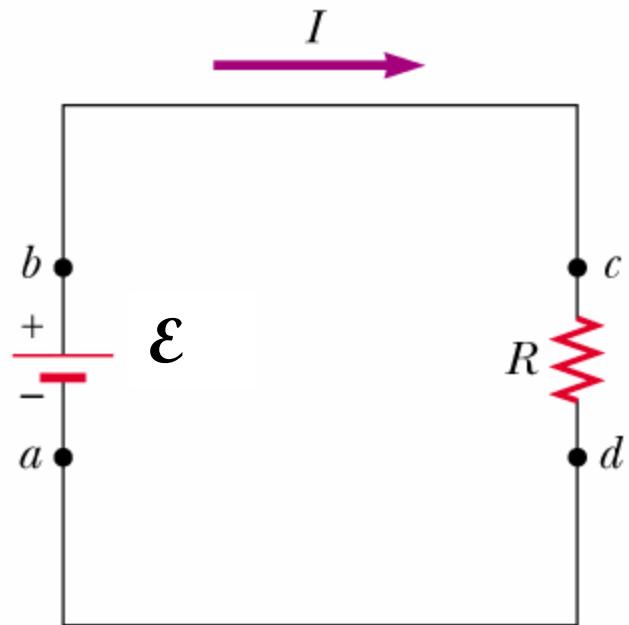

$$\mathcal{E} = I R$$

$$I = \frac{dq}{dt} = \frac{\mathcal{E}}{R}$$

Circuit with an emf and a capacitor:

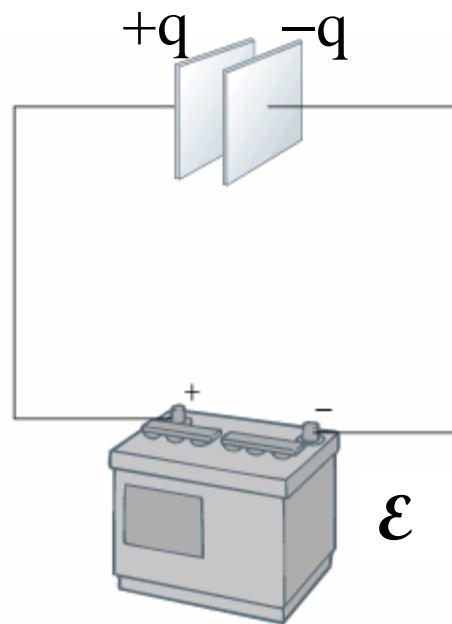


$$\mathcal{E} = \frac{q}{C}$$


$$q = \mathcal{E}C$$

Circuit containing capacitor and resistor --

Charging a capacitor:

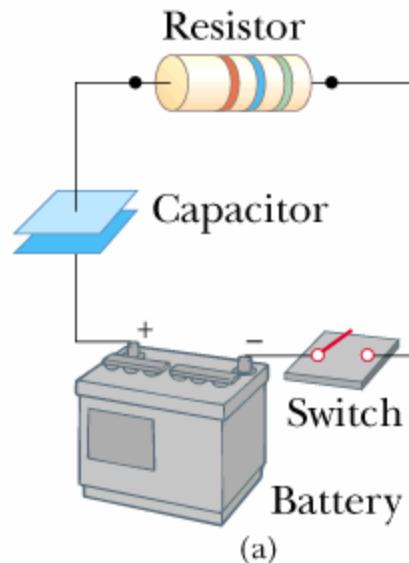


(a)

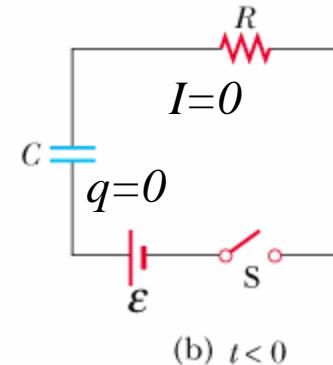

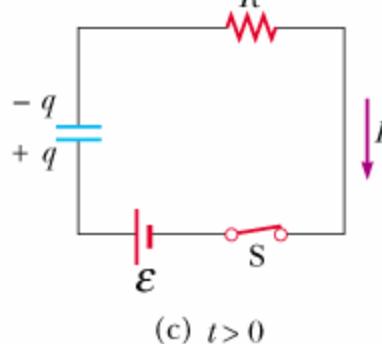(b)  $t < 0$

In a circuit, charge and current are related by :  $I = \frac{dq}{dt}$



(c)  $t > 0$

When the switch is closed :

$$\mathcal{E} - \frac{q}{C} - IR = 0 \quad \Rightarrow \quad \mathcal{E} - \frac{q}{C} - \frac{dq}{dt} R = 0$$

First order differential equation for charge  $q(t)$  and

$$\text{current } I(t) = \frac{dq}{dt}$$

$$\mathcal{E} - \frac{q}{C} - \frac{dq}{dt} R = 0$$

$$\text{initial condition : } q(t=0) = 0$$

solution :


$$q(t) = C\mathcal{E}\left(1 - e^{-t/(RC)}\right)$$

$$I(t) \equiv \frac{dq}{dt} = \frac{\mathcal{E}}{R} e^{-t/(RC)}$$


characteristic time constant  
for RC circuit

Solution:  $q(t) = C\mathcal{E}(1 - e^{-t/(RC)})$

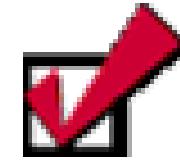Check:  $\mathcal{E} - \frac{q}{C} - \frac{dq}{dt}R = \mathcal{E} - \frac{C\mathcal{E}(1 - e^{-t/(RC)})}{C} - \frac{C\mathcal{E}e^{-t/(RC)}}{RC}R$   
 $= \mathcal{E} - \mathcal{E} + \mathcal{E}e^{-t/(RC)} - \mathcal{E}e^{-t/(RC)} = 0$



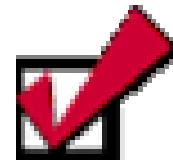
Initial condition:  $q(t=0) = C\mathcal{E}(1 - e^{-0/(RC)})$   
 $= C\mathcal{E}(1 - 1) = 0$



→ Mathematical analysis tells us that the solution is unique.

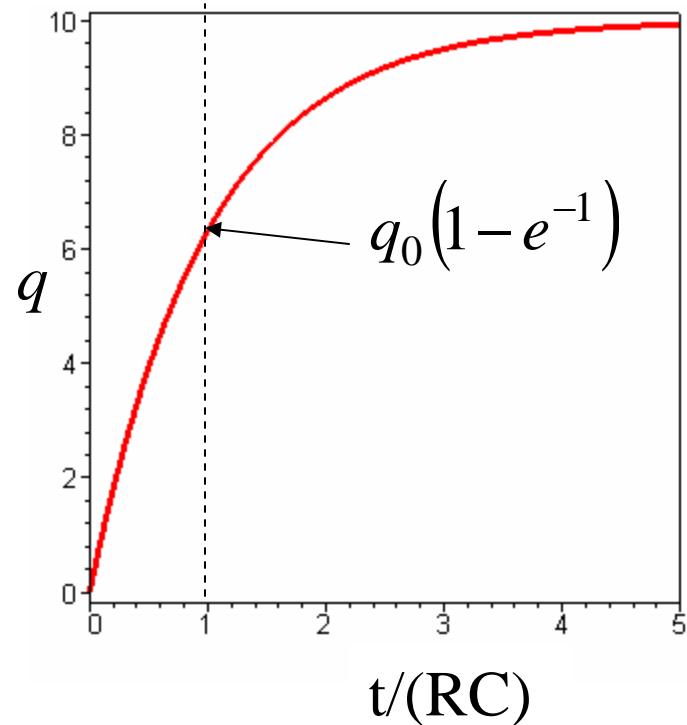
## Charge

$$q(t) = C\mathcal{E} \left( 1 - e^{-t/(RC)} \right)$$




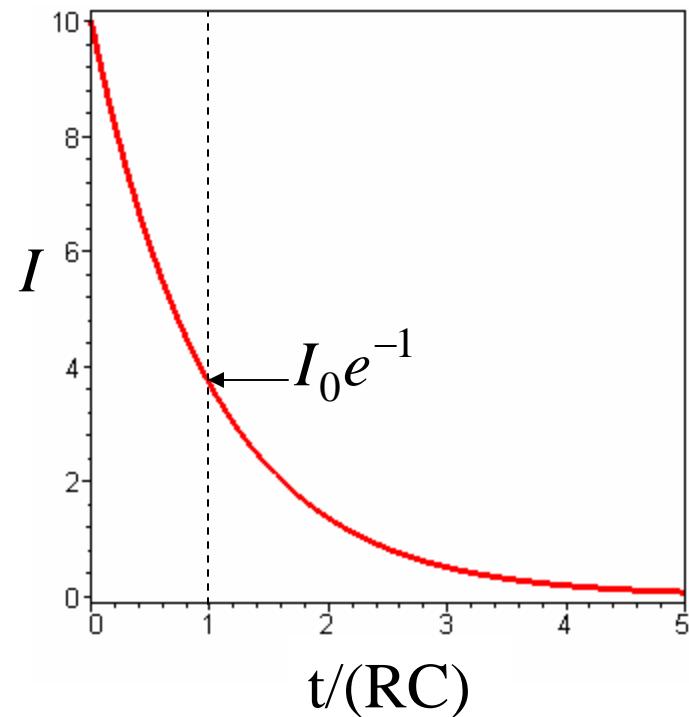
## Current


$$I(t) \equiv \frac{dq}{dt} = \frac{\mathcal{E}}{R} e^{-t/(RC)}$$



## Discharging a capacitor

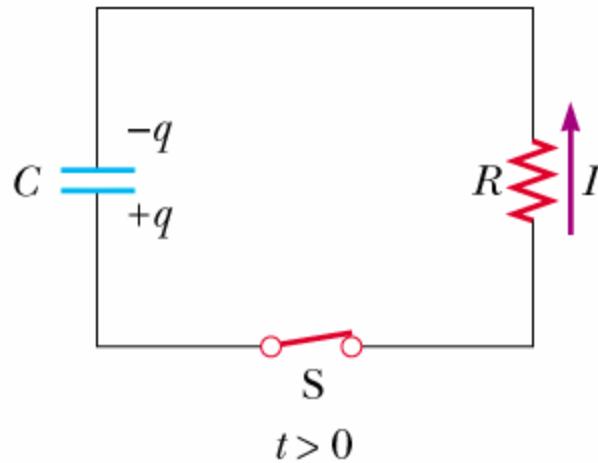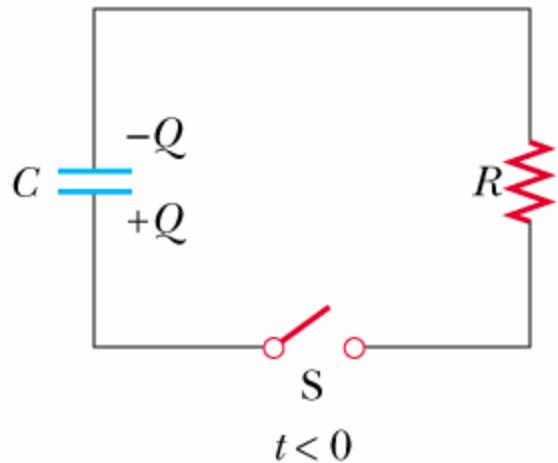

initial condition:  $q(t=0)=Q$

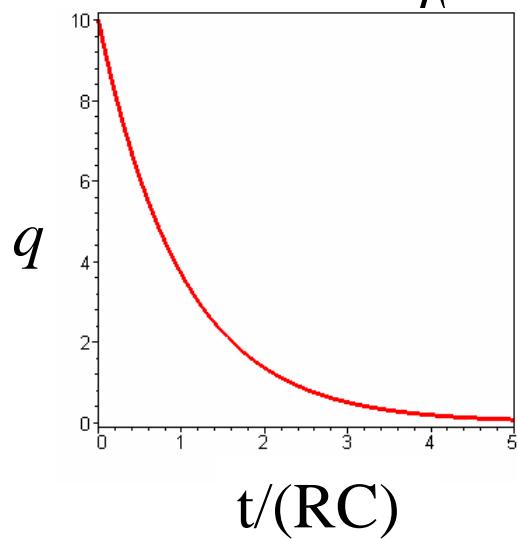


$$-\frac{q}{C} - IR = 0 \quad \Rightarrow \quad -\frac{q}{C} - \frac{dq}{dt} R = 0$$

solution :

$$q(t) = Q \left( e^{-t/(RC)} \right)$$

$$I(t) \equiv \frac{dq}{dt} = -\frac{Q}{RC} e^{-t/(RC)}$$

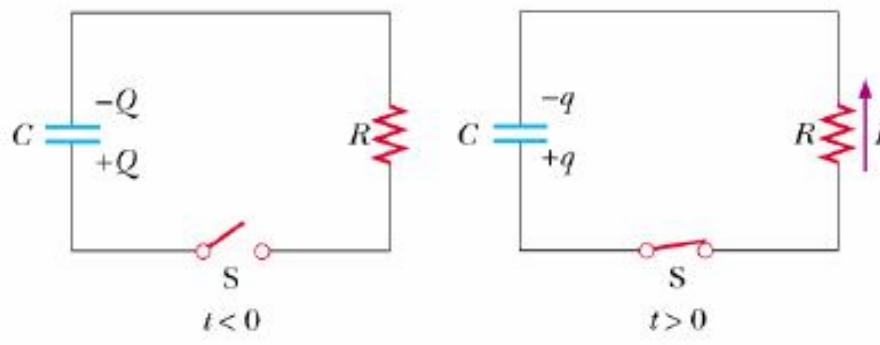Online Quiz for Lecture 9  
RC circuits -- Feb. 7, 2005



Consider the RC circuit shown in the diagram above. At  $t=0$ , the capacitor initially has a charge  $Q \rightarrow q(t=0)=Q$ . The capacitance is  $1 \times 10^{-6} \text{ F}$  and the resistance is  $R=5000\Omega$ .



1. How long will it take for the charge to be reduced to 37% of its initial value?  
 (A) 0.0001 s (B) 0.005 s (C) 0.023 s (D) 5 s (E) 23 s
2. How long will it take for the charge to be reduced to 1% of its initial value?  
 (A) 0.0001 s (B) 0.005 s (C) 0.023 s (D) 5 s (E) 23 s .

$$e^{-t/\tau} = 0.01$$

$$-t/\tau = \ln(0.01) = -4.605$$

$$\Rightarrow t = \tau \cdot (4.605) \approx 0.023$$
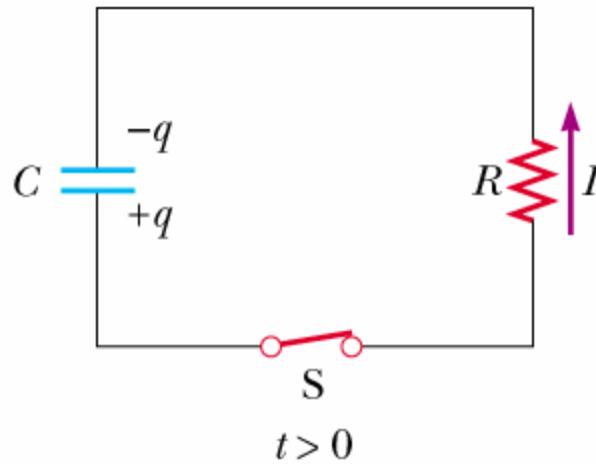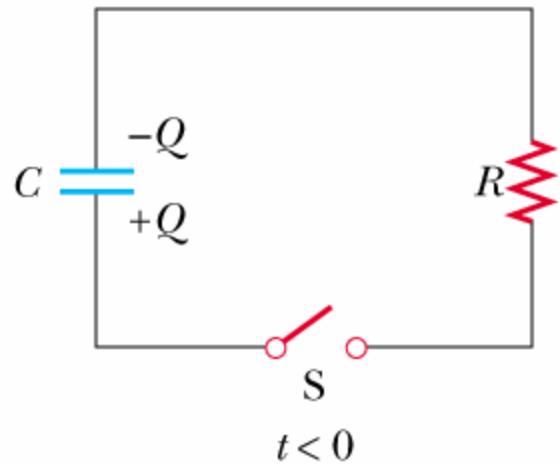
## RC circuit -- Discharging a capacitor through a resistor



initial condition:

$$q(t=0) = Q$$

after the switch is closed:

$$-\frac{q}{C} - IR = 0$$

$$\Rightarrow -\frac{q}{C} - \frac{dq}{dt} R = 0$$

Analysis:

$$-\frac{q}{C} - \frac{dq}{dt} R = 0$$

$$\frac{dq}{dt} = -\frac{1}{RC} q$$


$$\frac{dq}{q} = -\frac{1}{RC} dt$$

$$\ln\left(\frac{q(t)}{Q}\right) = -\frac{t}{RC}$$

Result :

$$q(t) = Q\left(e^{-t/(RC)}\right)$$
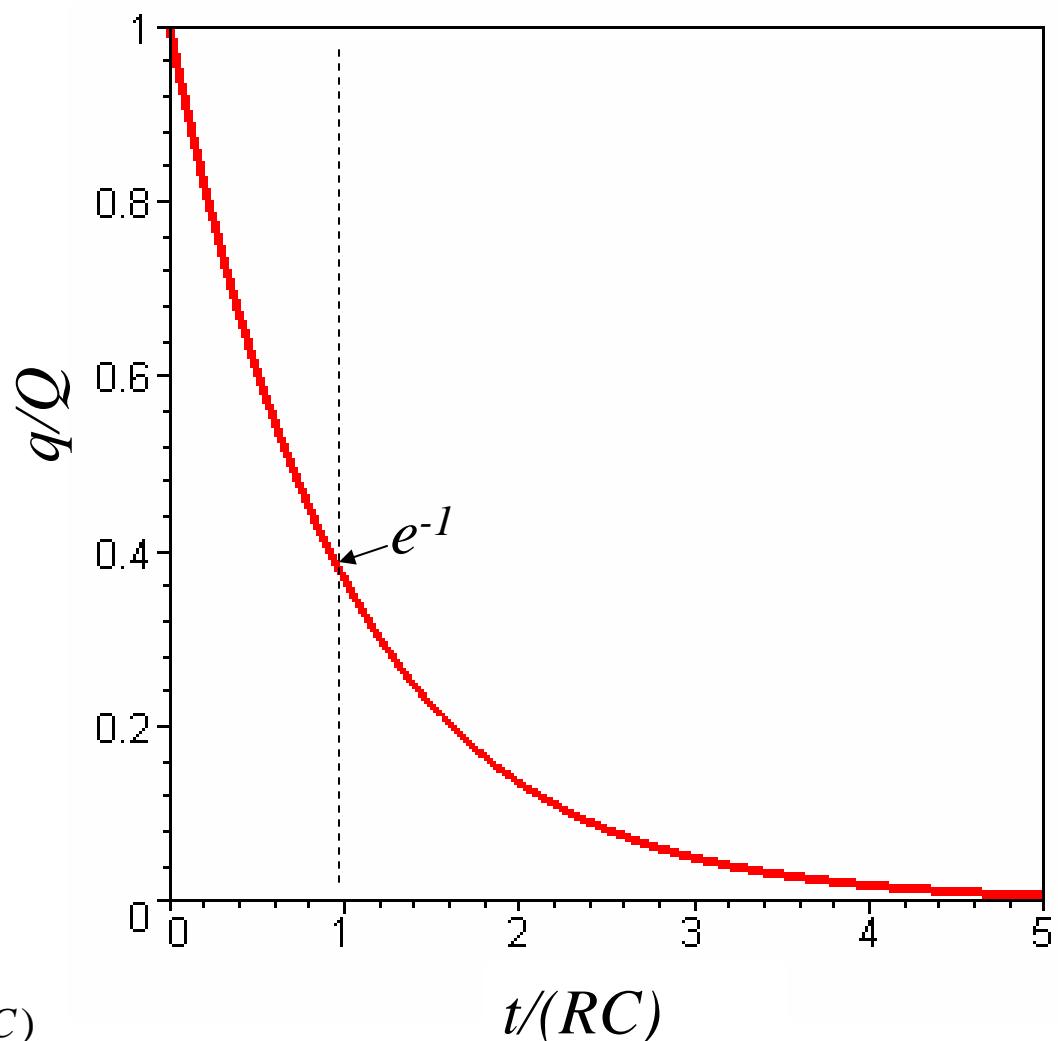
$$I(t) \equiv \frac{dq}{dt} = -\frac{Q}{RC} e^{-t/(RC)}$$



## General method for solving first-order linear differential equation

Assume we want to find  $q(t)$  in terms of constants  $A, B, C$ .

$$\alpha \frac{dq}{dt} + \beta q + \gamma = 0$$

Try solution form:  $q(t) = Xe^{Yt} + Z$

Substitute into equation:  $\alpha X(Y)e^{Yt} + \beta(Xe^{Yt} + Z) + \gamma = 0$

This must be true for all times  $t$ .

$$\beta Z + \gamma = 0 \quad \Rightarrow Z = -\gamma / \beta$$

$$\alpha XY + \beta X = 0 \quad \Rightarrow Y = -\beta / \alpha$$

X determined from initial conditions

If  $q(t=0) = Q \quad \Rightarrow X = Q + \gamma / \beta$

$$q(t) = Qe^{-\beta t / \alpha} + \frac{\gamma}{\beta} (e^{-\beta t / \alpha} - 1)$$

Extra credit:

Find several other examples of physical systems that obey a first order differential equation.

4. [HRW6 28.P.055.] In the circuit of Fig. 28-57,  $\mathcal{E} = 1.2 \text{ kV}$ ,  $C = 6.5 \mu\text{F}$ ,  $R_1 = R_2 = R_3 = 0.73 \text{ M}\Omega$ . With  $C$  completely uncharged, switch  $S$  is suddenly closed (at  $t = 0$ ).

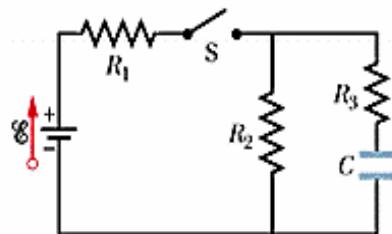


Figure 28-57.

Determine the current through each resistor for  
 $t = 0$

	A ( $I_1$ )
	A ( $I_2$ )
	A ( $I_3$ )

and  $t = \infty$

	A ( $I_1$ )
	A ( $I_2$ )
	A ( $I_3$ )