

PHY 114 A General Physics II
11 AM-12:15 PM TR Olin 101

Plan for Lecture 15 (Chapter 33):

Alternating current circuits

1.AC EMF

2.R, C, L behaviors in AC circuit

3.RLC circuits

3/22/2012 PHY 114 A Spring 2012 -- Lecture 15 1

Remember to send in your chapter reading questions...

W	3/22/2012	review	3/28/2012	review for exam
	02/28/2012	Exam		
11	03/01/2012	Magnetic fields	29.1-29.6	29.5-29.12,29.47
12	03/06/2012	Magnetic field sources	30.1-30.6	30.5,30.21,30.29
13	03/08/2012	Faraday's law	31.1-31.6	31.12,31.23,31.40
	03/13/2012	No class (Spring Break)		
	03/15/2012	No class (Spring Break)		
14	03/20/2012	Induction and AC circuits	32.1-32.6	32.4,32.20,32.43
15	03/22/2012	AC circuits	33.1-33.9	33.8,33.24,33.71
16	03/27/2012	Electromagnetic waves	34.1-34.3	34.3,34.10,34.13
17	03/29/2012	Electromagnetic waves	34.4-34.7	34.22,34.46,34.57
18	04/03/2012	Ray optics Evening exam	35.1-35.8	
19	04/05/2012	Image formation Evening exam	36.1-36.4	

3rd exam will be scheduled for evenings during the week of 4/2/2012

3/22/2012 PHY 114 A Spring 2012 -- Lecture 15 2

Homework hint:

In the circuit of Figure P32.48, the battery emf \mathcal{E} is 40 V, the resistance R is 100 Ω , and the capacitance C is 0.500 μF . The switch S is closed for a long time, and no voltage is measured across the capacitor. After the switch is opened, the potential difference across the capacitor reaches a maximum value of 150 V. What is the value of the inductance L ?

Figure P32.48

“The switch S is closed for a long time, and no voltage is measured across the capacitor.” Which of the following statements is false?

- The voltage across the inductor and the capacitor must always be the same.
- After a long time the current through the inductor is \mathcal{E}/R .
- After a long time the current through the resistor is \mathcal{E}/R .
- After a long time, the current through the inductor is 0.

3/22/2012 PHY 114 A Spring 2012 -- Lecture 15 3

Homework hint:

My Notes | SerPSE6, 32.P04

In the circuit of Figure P32.48, the battery emf \mathcal{E} is 40 V, the resistance R is 190 Ω , and the capacitance C is 0.500 μF . The switch S is closed for a long time, and no voltage is measured across the capacitor. After the switch is opened, the potential difference across the capacitor reaches a maximum value of 150 V. What is the value of the inductance L ?

Figure P32.48

After the switch S is opened ($t=0$) which of the following statements are true?

- The circuit is now an LC circuit with the initial condition that $Q(t=0)=C\mathcal{E}$.
- The circuit is now an LC circuit with the initial condition that $I(t=0)=\mathcal{E}/R$.
- The current will oscillate forever with an angular frequency of $\omega = 1/\sqrt{LC}$.

3/22/2012 PHY 114 A, Spring 2012 -- Lecture 15 4

DC - LRC circuit:

$$\mathcal{E} - \frac{Q}{C} - L \frac{dI}{dt} - RI = 0$$

$$L \frac{d^2Q}{dt^2} + R \frac{dQ}{dt} + \frac{1}{C} Q - \mathcal{E} = 0$$

Solution assuming $Q(t=0) = 0$:

$$Q(t) = C\mathcal{E} \left(1 - e^{-Rt/2L} \cos(\omega' t) \right)$$


$$\omega' = \sqrt{\frac{1}{LC} - \left(\frac{R}{2L}\right)^2}$$


3/22/2012 PHY 114 A, Spring 2012 -- Lecture 15 5

AC EMF source

$$\mathcal{E}(t) \equiv \Delta v(t) = \Delta V_{\max} \sin(\omega t) = \Delta V_{\max} \sin(2\pi f t)$$

3/22/2012 PHY 114 A, Spring 2012 -- Lecture 15 6

AC EMF source 
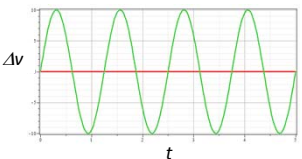
$$\mathcal{E}(t) \equiv \Delta v(t) = \Delta V_{\max} \sin(\omega t) = \Delta V_{\max} \sin(2\pi f t)$$


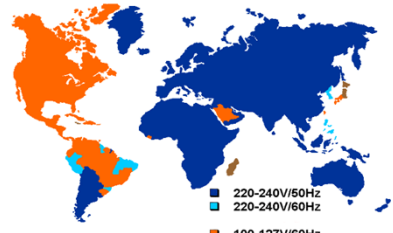
$$\langle \Delta v(t) \rangle = \int_0^{1/f} \Delta V_{\max} \sin(2\pi f t) dt = 0$$

$$\langle \Delta v(t) \rangle^2 = \int_0^{1/f} [\Delta V_{\max} \sin(2\pi f t)]^2 dt = \frac{1}{2} |\Delta V_{\max}|^2 \equiv |\Delta V_{\text{rms}}|^2$$



3/22/2012 PHY 114 A, Spring 2012 – Lecture 15 7

In US the standard wall voltage is $\Delta V_{\text{rms}} = 120 \text{ V}$ with $f = 60 \text{ Hz}$
 In Europe the standard wall voltage is $\Delta V_{\text{rms}} = 220 \text{ V}$ with $f = 50 \text{ Hz}$

Voltage standards throughout the world:
<http://users.telenet.be/worldstandards/electricity.htm#voltage>



3/22/2012 PHY 114 A, Spring 2012 – Lecture 15 8

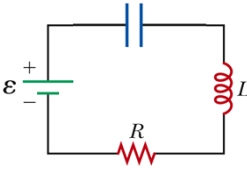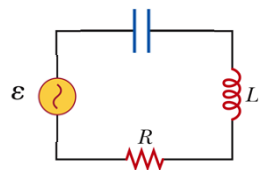DC - LRC circuit:  AC - LRC circuit: 

3/22/2012 PHY 114 A, Spring 2012 – Lecture 15 9

Which of the following statements most accurately reflect the relationships between the behaviors of LRC circuits with a DC versus an AC EMF source.

- A. The differential equations are different and the solutions are different.
- B. The differential equations are the same – but the solutions are different.
- C. The differential equations are the same – so the solutions have to be the same.


In fact: The DC solutions to the differential equations are generally valid representations of transient behaviors. Often we are interested in the “steady state” solutions in the presence of AC voltage sources.

3/22/2012

PHY 114 A, Spring 2012 – Lecture 15

10

AC EMF with resistor:

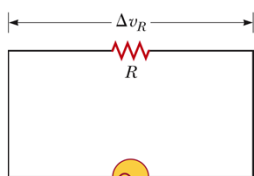

$$\Delta v - RI = 0$$

$$\Delta v = \Delta V_{\max} \sin \omega t$$

$$\Delta V_{\max} \sin(\omega t) - RI(t) = 0$$


$$\Rightarrow I(t) = \frac{\Delta V_{\max}}{R} \sin(\omega t)$$

3/22/2012

PHY 114 A, Spring 2012 – Lecture 15

11

AC EMF with capacitor:

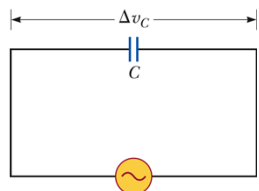

$$\Delta v - \frac{Q}{C} = 0$$

$$\Delta v = \Delta V_{\max} \sin \omega t$$

$$\Delta V_{\max} \sin(\omega t) - \frac{Q(t)}{C} = 0$$

$$\Rightarrow Q(t) = C \Delta V_{\max} \sin(\omega t)$$


$$\Rightarrow I(t) = \frac{dQ(t)}{dt} = \omega C \Delta V_{\max} \cos(\omega t)$$

3/22/2012

PHY 114 A, Spring 2012 – Lecture 15

12

AC EMF with inductor:

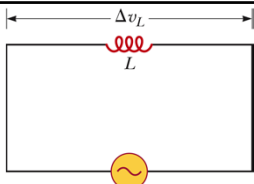

$$\Delta v - L \frac{dI}{dt} = 0$$

$$\Delta V_{\max} \sin(\omega t) - L \frac{dI(t)}{dt} = 0 \quad \Delta v = \Delta V_{\max} \sin \omega t$$

$$\Rightarrow \frac{dI(t)}{dt} = \frac{\Delta V_{\max}}{L} \sin(\omega t)$$

$$\Rightarrow I(t) = -\frac{\Delta V_{\max}}{\omega L} \cos(\omega t)$$

3/22/2012 PHY 114 A. Spring 2012 – Lecture 15 13

Summary of results for each circuit element:

General AC EMF of the form :

$$\Delta v(t) = \Delta V_{\max} \sin(\omega t - \phi)$$

With resistor only: $I(t) = \frac{\Delta V_{\max}}{R} \sin(\omega t - \phi)$


With capacitor only: $I(t) = \omega C \Delta V_{\max} \cos(\omega t - \phi)$

With inductor only: $I(t) = -\frac{\Delta V_{\max}}{\omega L} \cos(\omega t - \phi)$

3/22/2012 PHY 114 A. Spring 2012 – Lecture 15 14

Comment about phase factor ϕ :

Plots of $\sin(2\pi t + \phi)$

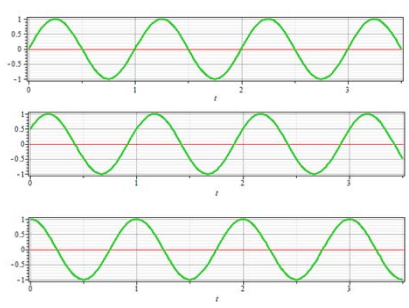

$\phi=0$

$\phi=0.5$

$\phi=1.57$

3/22/2012 PHY 114 A. Spring 2012 – Lecture 15 15

Series AC LRC circuit

$$\mathcal{E} - \frac{Q}{C} - L \frac{dI}{dt} - RI = 0$$


$$\mathcal{E} = \Delta V_{\max} \sin(\omega t)$$

Assume solution $I(t)$ to have the form :

$$I(t) = I_{\max} \sin(\omega t - \phi)$$


Declare success if :

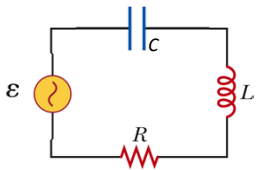- $I(t)$ satisfies differential equations
- I_{\max} has a consistent value
- ϕ has a consistent value



3/22/2012 PHY 114 A. Spring 2012 – Lecture 15 16

Series AC LRC circuit

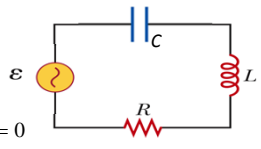

$$\Delta V_{\max} \sin(\omega t) - \frac{Q}{C} - L \frac{dI}{dt} - RI = 0$$


Assuming : $I(t) = I_{\max} \sin(\omega t - \phi)$

$$\Delta V_{\max} \sin(\omega t) + \frac{I_{\max} \cos(\omega t - \phi)}{\omega C} - \omega L I_{\max} \cos(\omega t - \phi) - R I_{\max} \sin(\omega t - \phi) = 0$$

→ Must be true at all t ; special values of I_{\max} and ϕ

3/22/2012 PHY 114 A. Spring 2012 – Lecture 15 17

Series AC LRC circuit

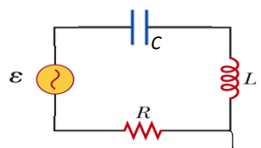

$$\Delta V_{\max} \sin(\omega t) - I_{\max} \left\{ \left(-\frac{1}{\omega C} + \omega L \right) \cos(\omega t - \phi) + R \sin(\omega t - \phi) \right\} = 0$$

$$\Delta V_{\max} \sin(\omega t) - I_{\max} \{ (-X_C + X_L) \cos(\omega t - \phi) + R \sin(\omega t - \phi) \} = 0$$

Some trig identities (see pg. A-12 of your text)

$$\sin(\alpha + \beta) = \sin \alpha \cos \beta + \cos \alpha \sin \beta$$

$$A \cos \beta + B \sin \beta = \sqrt{A^2 + B^2} \sin(\alpha + \beta)$$

if $\sin \alpha \equiv \frac{A}{\sqrt{A^2 + B^2}}$ and $\cos \alpha \equiv \frac{B}{\sqrt{A^2 + B^2}}$

3/22/2012 PHY 114 A. Spring 2012 – Lecture 15 18

$$\Delta V_{\max} \sin(\omega t) - I_{\max} \{(-X_C + X_L)\cos(\omega t - \phi) + R \sin(\omega t - \phi)\} = 0$$

$$\Delta V_{\max} \sin(\omega t) - I_{\max} \sqrt{(-X_C + X_L)^2 + R^2}$$

$$\times \left\{ \frac{(-X_C + X_L)}{\sqrt{(-X_C + X_L)^2 + R^2}} \cos(\omega t - \phi) + \frac{R}{\sqrt{(-X_C + X_L)^2 + R^2}} \sin(\omega t - \phi) \right\} = 0$$

Let $Z \equiv \sqrt{(-X_C + X_L)^2 + R^2}$

$$\sin \alpha \equiv \frac{(-X_C + X_L)}{\sqrt{(-X_C + X_L)^2 + R^2}}$$

$$\cos \alpha \equiv \frac{R}{\sqrt{(-X_C + X_L)^2 + R^2}}$$


$$\Delta V_{\max} \sin(\omega t) - I_{\max} Z \{ \sin \alpha \cos(\omega t - \phi) + \cos \alpha \sin(\omega t - \phi) \} = 0$$

$$\Delta V_{\max} \sin(\omega t) - I_{\max} Z \{ \sin(\alpha + \omega t - \phi) \} = 0$$

$$\Rightarrow \phi = \alpha \quad \Rightarrow \tan \phi = \frac{X_L - X_C}{R} \quad \Rightarrow I_{\max} = \frac{\Delta V_{\max}}{Z}$$

3/22/2012 PHY 114 A. Spring 2012 -- Lecture 15 19

Series AC LRC circuit

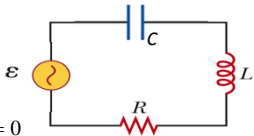

$$\Delta V_{\max} \sin(\omega t) - \frac{Q}{C} - L \frac{dI}{dt} - RI = 0$$

Assuming : $I(t) = I_{\max} \sin(\omega t - \phi)$


$$X_L \equiv \omega L \quad X_C \equiv \frac{1}{\omega C}$$

$$Z \equiv \sqrt{(X_L - X_C)^2 + R^2}$$

$$\tan \phi = \frac{X_L - X_C}{R} \quad I_{\max} = \frac{\Delta V_{\max}}{Z}$$

3/22/2012 PHY 114 A. Spring 2012 -- Lecture 15 20

Example AC LRC circuit:

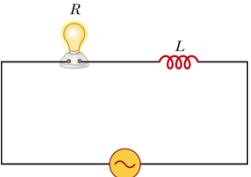


Consider the series resistor R and inductor L connected to an AC EMF. The voltage amplitude V_{\max} is held fixed while the frequency ω is varied. The bulb is brightest when

- ω is highest
- ω is lowest
- Bulb brightness is independent of ω

3/22/2012 PHY 114 A. Spring 2012 -- Lecture 15 21

Example AC LRC circuit:

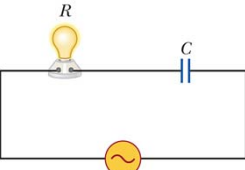


Consider the series resistor R and capacitor C connected to an AC EMF. The voltage amplitude V_{\max} is held fixed while the frequency ω is varied. The bulb is brightest when

- ω is highest
- ω is lowest
- Bulb brightness is independent of ω

3/22/2012 PHY 114 A. Spring 2012 – Lecture 15 22

Example AC LRC circuit:

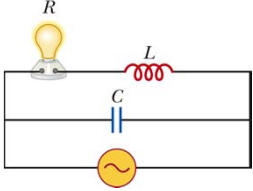

Consider the series resistor R and capacitor C connected to an AC EMF. The voltage amplitude V_{\max} is held fixed while the frequency ω is varied. The bulb is brightest when

- ω is highest
- ω is lowest
- Bulb brightness is independent of ω

3/22/2012 PHY 114 A. Spring 2012 – Lecture 15 23

Power in an AC circuit

$$P = I\Delta v = I_{\max} \sin(\omega t - \phi) \Delta V_{\max} \sin(\omega t)$$

$$= \frac{(\Delta V_{\max})^2}{Z} \sin(\omega t - \phi) \sin(\omega t)$$

$$= \frac{(\Delta V_{\max})^2}{Z} (\sin^2(\omega t) \cos \phi - \cos(\omega t) \sin(\omega t) \sin \phi)$$

$$\langle P \rangle_{\text{avg}} = \frac{1}{2} \frac{(\Delta V_{\max})^2}{Z} \cos \phi$$

Note :

$$\int_0^{2\pi/\omega} \sin^2(\omega t) dt = \frac{1}{2} \int_0^{2\pi/\omega} \sin(\omega t) \cos(\omega t) dt = 0$$

3/22/2012 PHY 114 A. Spring 2012 – Lecture 15 24

Power in an AC circuit -- continued

$$\langle P \rangle_{avg} = \frac{1}{2} \frac{(\Delta V_{max})^2}{Z} \cos \phi$$

Recall : $Z \equiv \sqrt{(X_L - X_C)^2 + R^2}$

$$\cos \phi = \frac{R}{\sqrt{(X_L + X_C)^2 + R^2}} = \frac{R}{Z}$$

$$\Rightarrow \langle P \rangle_{avg} = \frac{1}{2} \left(\frac{\Delta V_{max}}{Z} \right)^2 R = \frac{1}{2} (I_{max})^2 R$$

3/22/2012 PHY 114 A Spring 2012 -- Lecture 15 25

Frequency dependence of impedance in AC circuit

For pure LC circuit, we found a resonance frequency


$$\omega_0 = \sqrt{\frac{1}{LC}}$$

$$Z = \sqrt{(X_L - X_C)^2 + R^2} = \sqrt{\left(\omega L - \frac{1}{\omega C}\right)^2 + R^2}$$

$$Z = \sqrt{\omega^2 L^2 \left(1 - \frac{\omega_0^2}{\omega^2}\right)^2 + R^2}$$

$$\langle P \rangle_{avg} = \frac{1}{2} \left(\frac{\Delta V_{max}}{Z} \right)^2 R = \frac{1}{2} (\Delta V_{max})^2 \frac{R}{\omega^2 L^2 \left(1 - \frac{\omega_0^2}{\omega^2}\right)^2 + R^2}$$

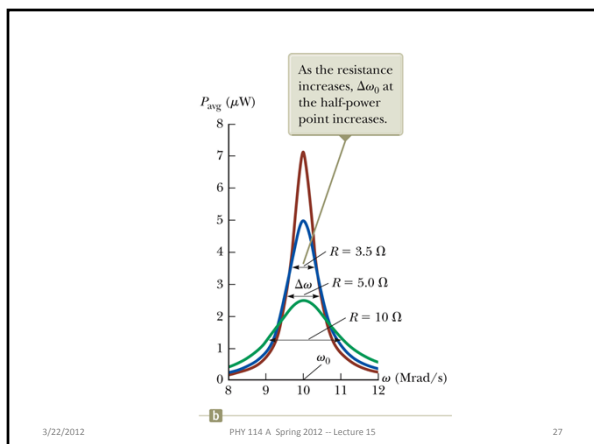3/22/2012 PHY 114 A Spring 2012 -- Lecture 15 26



DC - LRC circuit:

AC - LRC circuit:

Solution assuming $Q(t=0) = 0$:

$$Q(t) = C\mathcal{E}(1 - e^{-Rt/2L} \cos(\omega't))$$

$$\omega' = \sqrt{\frac{1}{LC} - \left(\frac{R}{2L}\right)^2}$$

"Steady-state" solution for $\mathcal{E} = \Delta V_{\max} \sin(\omega t)$

$$I(t) = \frac{\Delta V_{\max}}{Z} \sin(\omega t - \phi)$$

$$X_L = \omega L; \quad X_C = \frac{1}{\omega C}; \quad \tan \phi = \frac{X_L - X_C}{R}$$

$$Z = \sqrt{(X_L - X_C)^2 + R^2}$$

3/22/2012 PHY 114 A, Spring 2012 -- Lecture 15 28

AC transformer devices:

An alternating voltage Δv_1 is applied to the primary coil, and the output voltage Δv_2 is across the resistor of resistance R_L .

Faraday's law for Δv_1 :

$$\Delta v_1 = -N_1 \frac{d\Phi_B}{dt}$$

Faraday's law for Δv_2 :

$$\Delta v_2 = -N_2 \frac{d\Phi_B}{dt}$$

To a good approximation, $\frac{d\Phi_B}{dt}$ is the same for 1 and 2 :

$$\Rightarrow \Delta v_2 = \frac{N_2}{N_1} \Delta v_1$$

3/22/2012 PHY 114 A, Spring 2012 -- Lecture 15 29

AC transformer example:

$$\Delta v_2 = \frac{N_2}{N_1} \Delta v_1$$

Both Δv_1 and Δv_2 are oscillating in time; applying the equality to the RMS amplitudes,

we can determine N_2 / N_1 need for $\frac{V_{rms 2}}{V_{rms 1}} = \frac{12}{120}$:

$$\frac{N_2}{N_1} = \frac{V_{rms 2}}{V_{rms 1}} = \frac{1}{10}$$

If Δv_1 were a DC voltage source:

- The transformer would work in the same way.
- The transformer would not work at all.

3/22/2012 PHY 114 A, Spring 2012 -- Lecture 15 30
