

PHY 114 A General Physics II
11 AM-12:15 PM TR Olin 101

Plan for Lecture 8 (Chapter 28):

- 1. Direct-current circuits**
- 2. Voltage and resistor circuits**
- 3. Kirchoff's rules**

2/16/2012 PHY 114 A Spring 2012 -- Lecture 8 1

2	01/24/2012	Electric field	23.4-23.7	23.22, 23.20, 23.61a	01/26/2012
3	01/26/2012	Gauss's Law	24.1-24.3	24.22a, 24.23, 24.40	01/31/2012
4	01/31/2012	Electric potential	25.1-25.4	25.12, 25.23, 25.34, 25.01	02/02/2012
5	02/02/2012	Electric potential	25.5-25.8	(Review for exam)	
	02/07/2012	Exam			
6	02/09/2012	Capacitance and dielectrics	26.1-26.7	26.4, 26.13, 26.30	02/14/2012
7	02/14/2012	Current and resistance	27.1-27.6	27.3, 27.12, 27.23	02/16/2012
8	02/16/2012	Direct current circuits	28.1-28.2	28.3, 28.7, 28.19	02/21/2012
9	02/21/2012	Direct current circuits	28.3-28.5	28.23, 28.25, 28.34	02/23/2012
10	02/23/2012	Review	26.1-28.5	(Review for exam)	
	02/28/2012	Exam			
11	03/01/2012	Magnetic fields	29.1-29.6	29.5, 29.12, 29.47	03/06/2012
12	03/06/2012	Magnetic field sources	30.1-30.6		
13	03/08/2012	Faraday's law	31.1-31.5		
	03/13/2012	No class (Spring Break)			

Remember to send in your chapter reading questions...

2/16/2012 PHY 114 A Spring 2012 -- Lecture 8 2

Comment on Direct current versus Alternating current
<http://www.pbs.org/wgbh/amex/edison/sfeature/acdc.html>

Example – Li ion rechargeable battery
<http://electronics.howstuffworks.com/everyday-tech/lithium-ion-battery1.htm>

Lithium-ion rechargeable battery
Discharge mechanism

(Polymer battery: gel polymer electrolyte) ©2006 howstuffworks

Lithium-ion rechargeable battery
Charge mechanism

(Polymer battery: gel polymer electrolyte) ©2006 howstuffworks

2/16/2012 PHY 114 A Spring 2012 -- Lecture 8 3

Switch open, no current flowing, battery storing energy

Switch closed, current flowing, battery discharging

2/16/2012 PHY 114 A Spring 2012 – Lecture 8 4

Equivalent circuit for \mathcal{E}

$$\mathcal{E} - Ir - IR = 0$$

$$I = \frac{\mathcal{E}}{r + R}$$

$\mathcal{E} = 12\text{V}$, $r = 0.1\Omega$, $R = 9.9\Omega$;
what is ΔV ?

A. $\Delta V = \mathcal{E}$
B. $\Delta V < \mathcal{E}$
C. $\Delta V > \mathcal{E}$

2/16/2012 PHY 114 A Spring 2012 – Lecture 8 5

Resistors in series:

A pictorial representation of two resistors connected in series to a battery

A circuit diagram showing the two resistors connected in series to a battery

$$\Delta V - IR_1 - IR_2 = 0 \quad I = \frac{\Delta V}{R_1 + R_2} \quad R_{\text{series}} = R_1 + R_2$$

2/16/2012 PHY 114 A Spring 2012 – Lecture 8 6

Resistors in parallel

A pictorial representation of two resistors connected in parallel to a battery

A circuit diagram showing the two resistors connected in parallel to a battery

$$\Delta V - I_1 R_1 = 0$$

$$\Delta V - I_2 R_2 = 0$$

$$I = I_1 + I_2 = \frac{\Delta V}{R_1} + \frac{\Delta V}{R_2}$$

$$\Delta V = I \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}} \equiv IR_{Parallel}$$

$$R_{Parallel} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}}$$

2/16/2012
PHY 114 A Spring 2012 – Lecture 8
7

Examples: $R_1=1\Omega, R_2=100\Omega, \Delta V=100V$

$$\Delta V - IR_1 - IR_2 = 0$$

$$I = \frac{\Delta V}{R_1 + R_2} = \frac{100}{101} = 0.99A$$

$$\Delta V_1 = IR_1 = 0.99V$$

$$\Delta V_2 = IR_2 = 99.01V$$

$$\Delta V - I_1 R_1 = 0$$

$$\Delta V - I_2 R_2 = 0$$

$$I_1 = \frac{\Delta V}{R_1} = \frac{100}{1} = 100A$$

$$I_2 = \frac{\Delta V}{R_2} = \frac{100}{100} = 1A$$

$$I = I_1 + I_2 = 101A$$

2/16/2012
PHY 114 A Spring 2012 – Lecture 8
8

Circuit analysis – Kirchhoff's rules


Conservation of charge (current) at a junction:

$$\sum_{junction} I = 0$$

$$I_1 - I_2 - I_3 = 0$$

2/16/2012
PHY 114 A Spring 2012 – Lecture 8
9

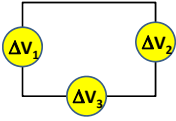Circuit analysis – Kirchoff's rules
Conservation of potential around a closed circuit:



Sign conventions: $\Delta V = V_b - V_a$

a \xrightarrow{I} b
 $\Delta V = -IR$

b \xleftarrow{I} a
 $\Delta V = +IR$


c $\xrightarrow{\mathcal{E}}$ b
 $\Delta V = +\mathcal{E}$

d $\xleftarrow{\mathcal{E}}$ a
 $\Delta V = -\mathcal{E}$

$\sum_{\text{closed loop}} \Delta V = 0$
 $\Delta V_1 + \Delta V_2 + \Delta V_3 = 0$

2/16/2012 PHY 114 A Spring 2012 – Lecture 8 10

Example:

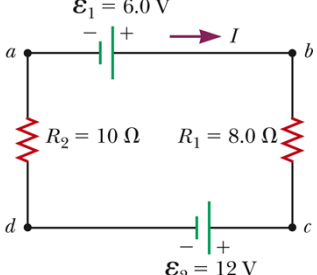

$\mathcal{E}_1 = 6.0 \text{ V}$

$\mathcal{E}_2 = 12 \text{ V}$


$R_2 = 10 \Omega$ $R_1 = 8.0 \Omega$

$\mathcal{E}_1 - IR_1 - \mathcal{E}_2 - IR_2 = 0$
Solve for I :
 $I = \frac{\mathcal{E}_1 - \mathcal{E}_2}{R_1 + R_2} = \frac{6 - 12}{8 + 10} = -0.33 \text{ A}$

$I < 0$ means:
A. The circuit is wrong (cannot exist or will blow up).
B. The current flows opposite the arrow.

2/16/2012 PHY 114 A Spring 2012 – Lecture 8 11

Example:

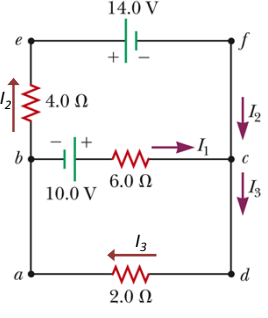

14.0 V

10.0 V

4.0Ω 6.0Ω 2.0Ω

$I_1 + I_2 = I_3$

$-14 - 2I_3 - 4I_2 = 0$
 $10 - 6I_1 - 2I_3 = 0$

$I_1 = 2 \text{ A}$
 $I_2 = -3 \text{ A}$
 $I_3 = -1 \text{ A}$

2/16/2012 PHY 114 A Spring 2012 – Lecture 8 12

How to measure current

Inside ammeter:

$$I = I_1 + I_2$$

$$R_{eq} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}}$$

$I_1 \equiv$ "shunt" current; $R_1 \ll R_2$
 $I_2 \equiv$ device current; $I_2 \ll I_1$

2/16/2012 PHY 114 A Spring 2012 -- Lecture 8 13

Suppose that :

$I = 10\text{ A}$, $R_1 = 0.01\Omega$, $R_2 = 100\Omega$

$$I_2 = \frac{I}{1 + \frac{R_2}{R_1}} = \frac{10}{10001}\text{ A} = 0.001\text{ A}$$

➔ Current that drives measurement device.

2/16/2012 PHY 114 A Spring 2012 -- Lecture 8 14


What if the ammeter were connected in parallel to the wire?
 (Assume that the wire resistance is $R_w=0.001\Omega$.)

A. The measurement would be identical to series result.
 B. The measurement would be less than the series result.
 C. The measurement would be greater than the series result.


$$I_2 = \frac{I}{1 + \frac{R_2}{R_1} + \frac{R_2}{R_w}} = \frac{10}{110001}\text{ A} = 0.0001\text{ A}$$

2/16/2012 PHY 114 A Spring 2012 -- Lecture 8 15

How to measure voltage

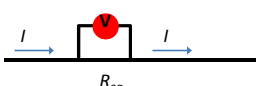

Total equivalent circuit:

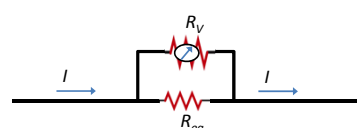


$$I_V R_V = \frac{I R_{eq}}{1 + \frac{R_{eq}}{R_V}}$$

⇒ Works well if $R_V \gg R_{eq}$

2/16/2012 PHY 114 A Spring 2012 – Lecture 8 16

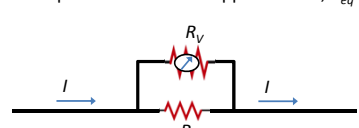
Total equivalent circuit: Suppose $I=10A$, $R_{eq}=10\Omega$, $R_V=100\Omega$



$$I_V R_V = \frac{10 \times 100}{1 + \frac{10}{100}} = 909.1$$

$$\frac{I R_{eq} - I_V R_V}{I R_{eq}} = 9\%$$

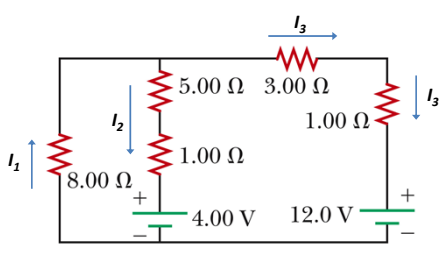2/16/2012 PHY 114 A Spring 2012 – Lecture 8 17



3 unknowns → need 3 equations

$$I_1 = I_2 + I_3$$

$$-8I_1 - 6I_2 - 4 = 0$$

$$-4I_3 - 12 - 8I_1 = 0$$

$$-4I_3 - 12 + 4 + 6I_2 = 0$$

2/16/2012 PHY 114 A Spring 2012 – Lecture 8 18
