


PHY 114 A General Physics II
11 AM-12:15 PM TR Olin 101

Plan for Lecture 9 (Chapter 28):

- 1. Direct-current circuits continued**
- 2. Voltage, resistor, and capacitor circuits**

5	02/02/2012	Electric potential	25.5-25.8	(Review for exam)	
	02/07/2012	Exam			
6	02/09/2012	Capacitance and dielectrics	26.1-26.7	26.4.26.13.26.30	02/14/2012
7	02/14/2012	Current and resistance	27.1-27.6	27.3.27.12.27.29	02/16/2012
8	02/16/2012	Direct current circuits	28.1-28.2	28.3.28.7.28.19	02/21/2012
	02/21/2012	Direct current circuits	28.3-28.5	28.23.28.25.28.34	02/23/2012
10	02/23/2012	Review	26.1-28.5	(Review for exam)	
	02/28/2012	Exam			
11	03/01/2012	Magnetic fields	29.1-29.6	29.5.29.12.29.47	03/06/2012
12	03/06/2012	Magnetic field sources	30.1-30.6		
13	03/08/2012	Faraday's law	31.1-31.5		
	03/13/2012	<i>No class (Spring Break)</i>			
	03/15/2012	<i>No class (Spring Break)</i>			
14	03/20/2012	Induction and AC circuits	32.1-32.6		


Remember to send in your chapter reading questions...

Professor George Holzwarth (gholz@wfu.edu)
will administer the exam on 2/28/2012
and will lecture on magnetic fields, electric
motors, etc. on 3/1/2012.

Circuit diagram:

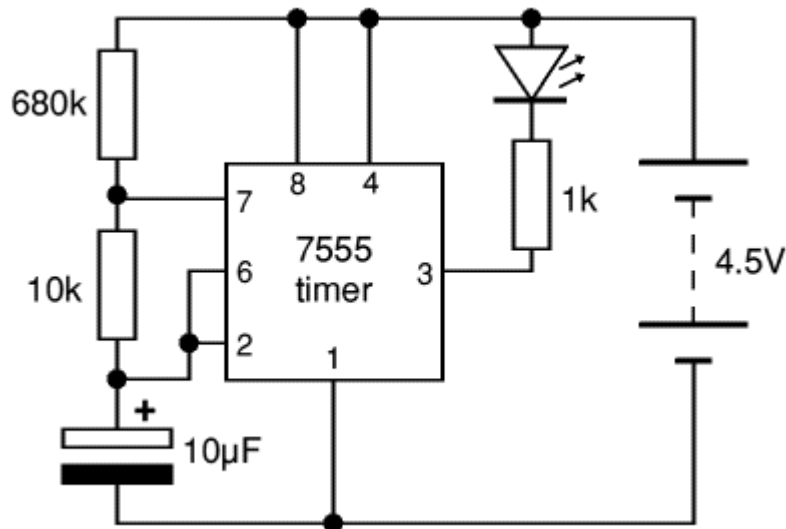
Example project from web page

<http://www.kpsec.freeuk.com/projects/dummy.htm>



From webassign:

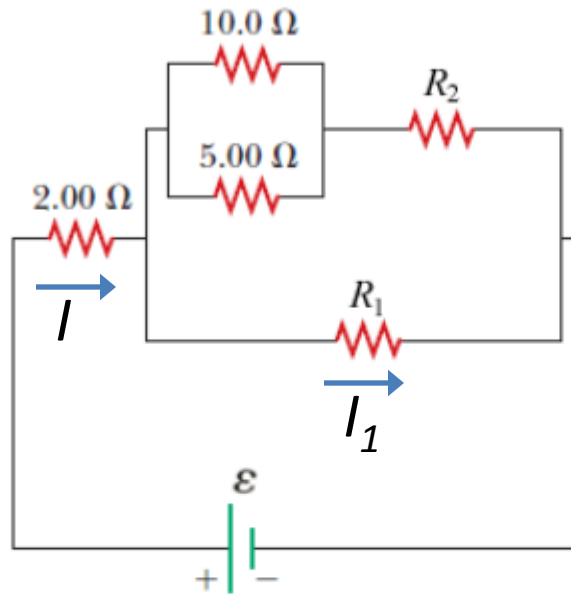Consider the circuit shown in the figure below. (Let $R_1 = 3.00 \, \Omega$, $R_2 = 4.00 \, \Omega$, and $\mathcal{E} = 6.00 \, \text{V}$.)



(a) Find the voltage across R_1 .

V

(b) Find the current in R_1 .

A

$$\mathcal{E} - 2I - R_1 I_1 = 0$$


$$\Delta V_1 = R_1 I_1 = \mathcal{E} - 2I$$

among the many ways to find I :


$$I = \frac{\mathcal{E}}{R_{eq}}$$

Circuits involving Voltage, Capacitance, and Resistance


Open switch
 → no charge
 or current

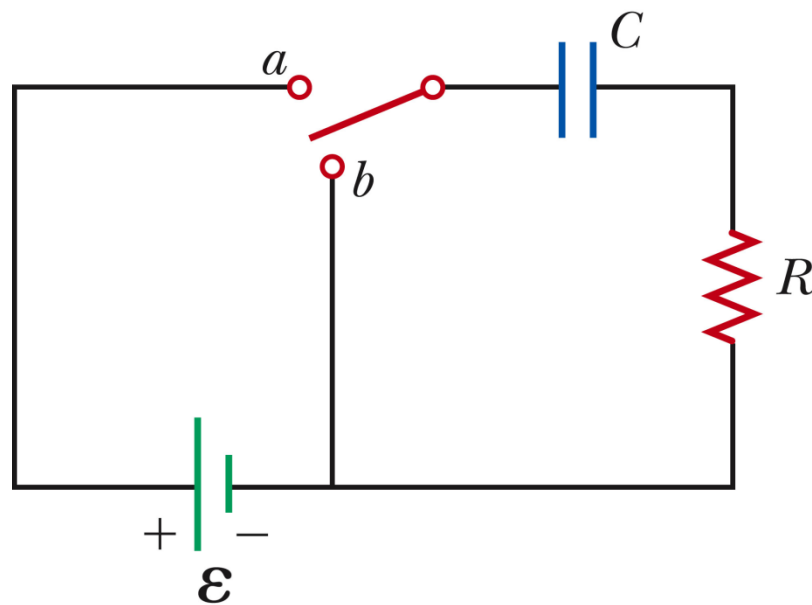


Switch closed
 → VCR circuit

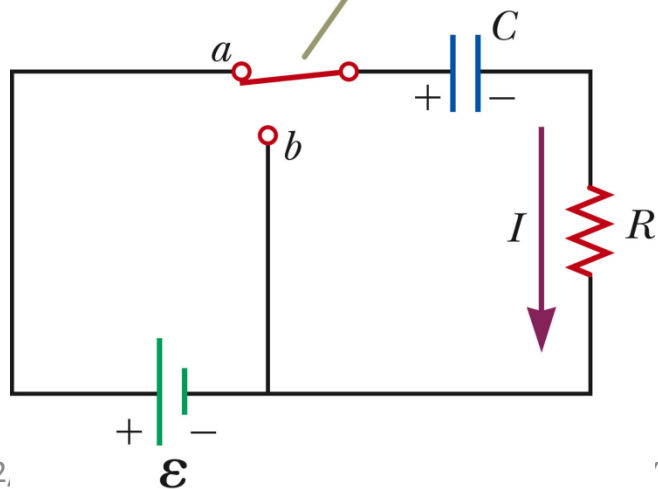

Switch closed
 → RC circuit

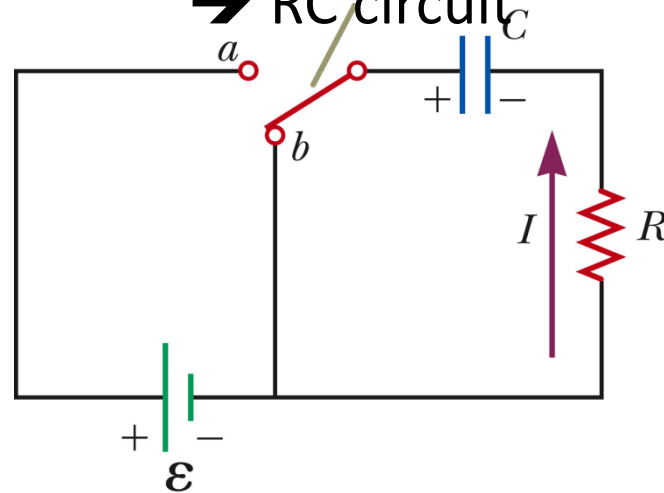

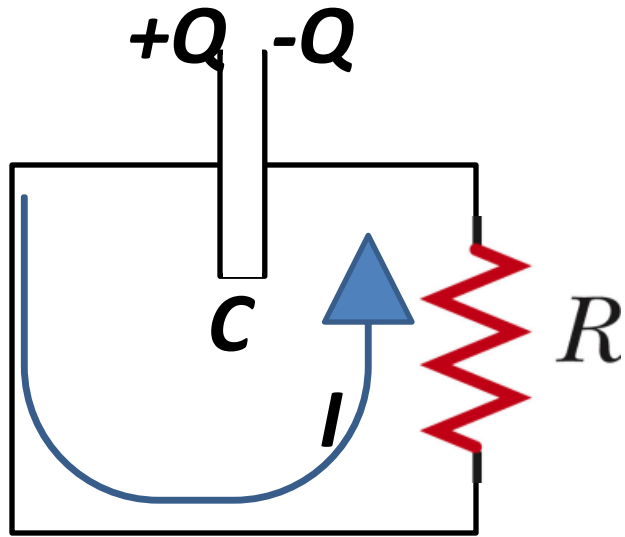

$$-\frac{Q}{C} - IR = 0$$

$$I = \frac{dQ}{dt}$$

$$-\frac{Q}{C} - \frac{dQ}{dt} R = 0$$

$$\frac{dQ}{dt} = -\frac{1}{RC} Q$$

What are the units of RC?

- A. Seconds
- B. Cycles per second
- C. Meters
- D. Coulombs
- E. Volts

Simple rate equation for growth :

$$\frac{dM}{dt} = rM$$

$$\frac{dM}{dt} = \text{rate of accumulation of money}$$


r = rate of increase

$M = M(t)$ = money at time t

Analysis:

$$\frac{dM}{dt} = rM \quad \Rightarrow \quad \frac{dM}{M} = d \ln(M) = r dt$$

$$\ln(M) \Big|_{M_0}^M = rt \Big|_{t_0}^t \quad \Rightarrow \quad M(t) = M_0 e^{r(t-t_0)}$$

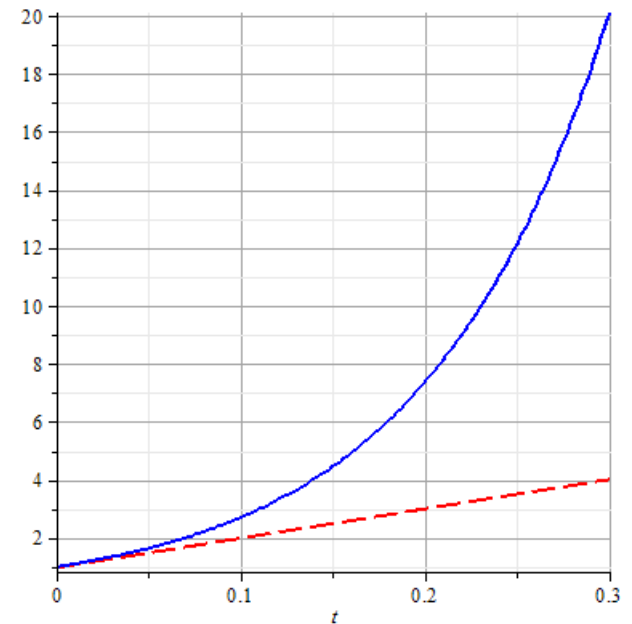

Simple rate equation for decrease :

$$\frac{dM}{dt} = -rM$$

$$\frac{dM}{dt} = \text{rate of accumulation of money}$$


r = rate of decrease


$M = M(t)$ = money at time t

Analysis :

$$\frac{dM}{dt} = -rM \quad \Rightarrow \quad \frac{dM}{M} = d \ln(M) = -r dt$$


$$\ln(M) \Big|_{M_0}^M = -rt \Big|_{t_0}^t \quad \Rightarrow \quad M(t) = M_0 e^{-r(t-t_0)}$$

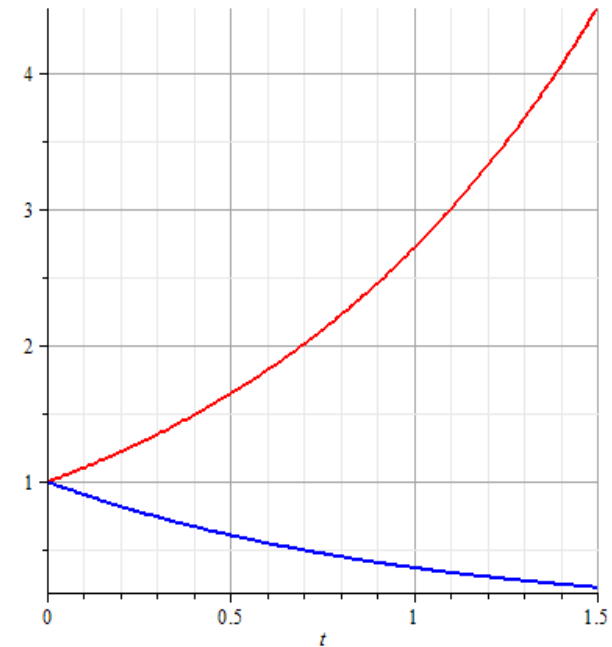

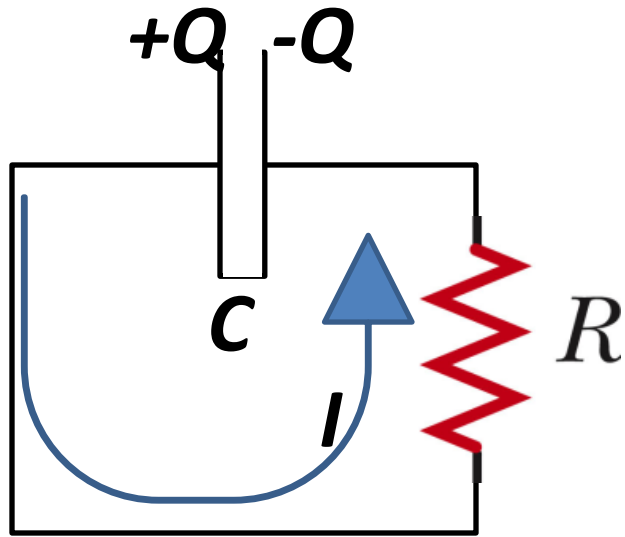


$$\frac{dQ}{dt} = -\frac{1}{RC}Q = -\frac{1}{\tau}$$

$$Q(t) = Q_0 e^{-(t-t_0)/\tau}$$

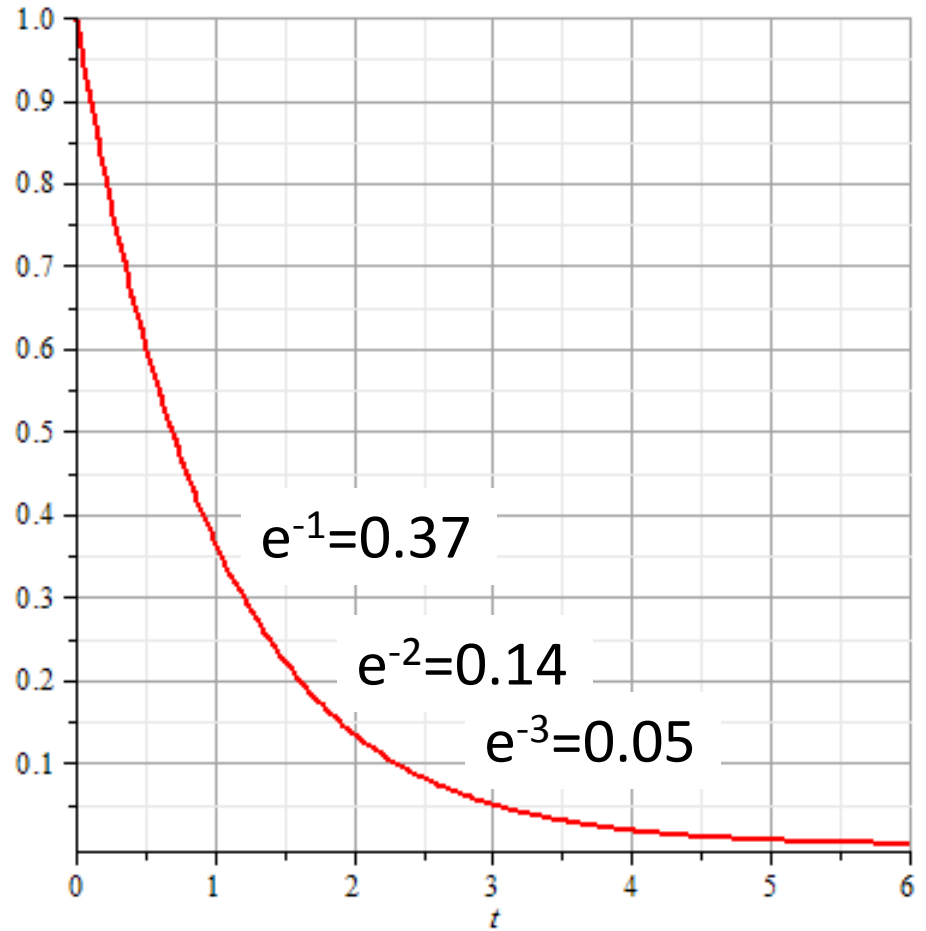

Charging capacitor:

Switch closed at $t=0$; $Q(t=0)=0$

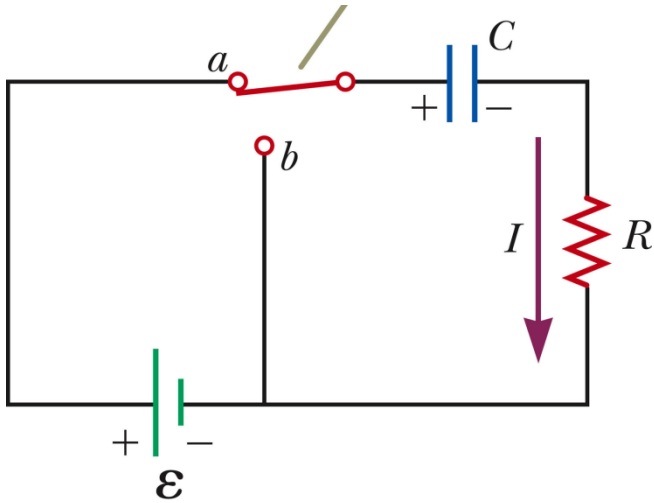


$$\epsilon - \frac{Q}{C} - IR = 0 = \epsilon - \frac{Q}{C} - \frac{dQ}{dt} R$$


$$\frac{dQ}{dt} = -\frac{1}{RC} (Q - C\epsilon) \equiv -\frac{1}{\tau} (Q - C\epsilon)$$

Charging capacitor:


Switch closed at $t=0$; $Q(t=0)=0$

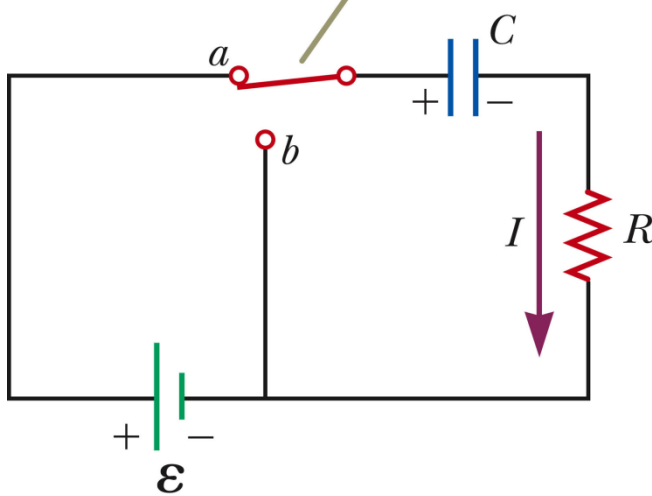
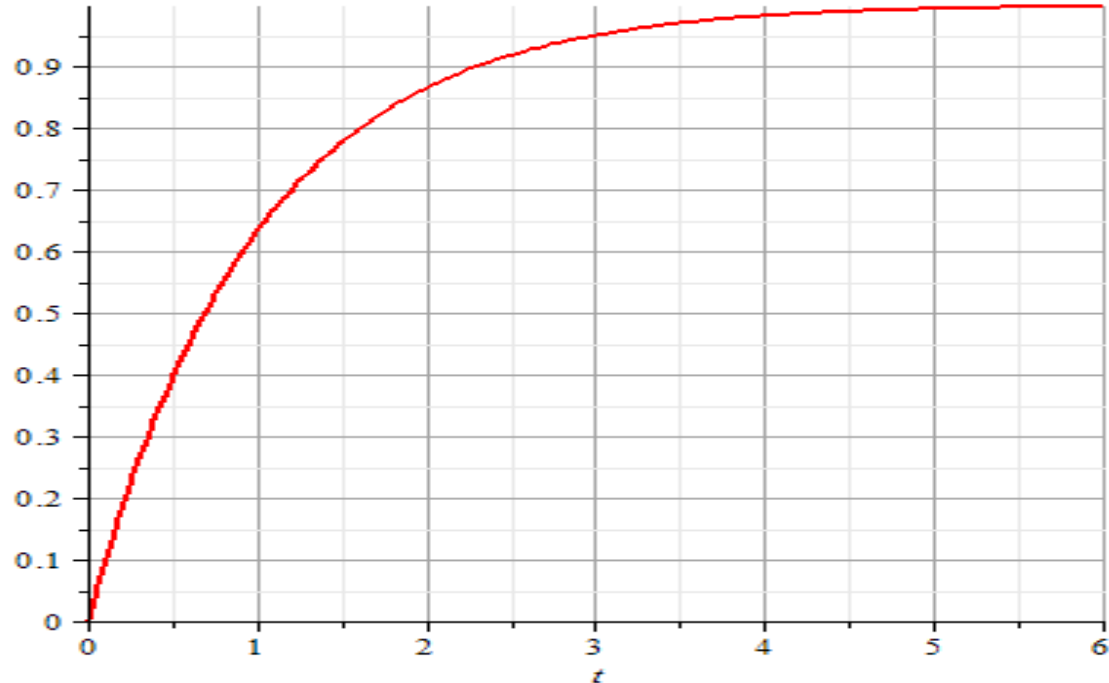
$$\frac{dQ}{dt} = -\frac{1}{RC}(Q - C\mathcal{E}) \equiv -\frac{1}{\tau}(Q - C\mathcal{E})$$
$$Q(t) = C\mathcal{E}(1 - e^{-t/\tau})$$




Discharging capacitor

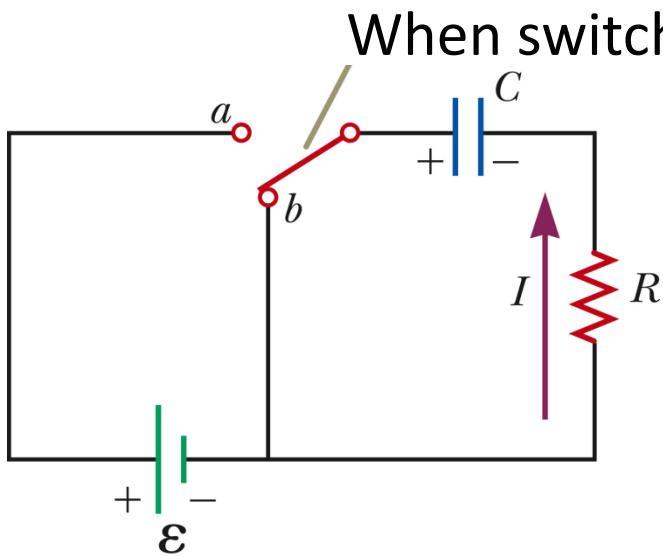



$$\frac{dQ}{dt} = -\frac{1}{RC}Q = -\frac{1}{\tau}Q$$

$$Q(t) = C\mathcal{E}e^{-(t-t_c)/\tau}$$

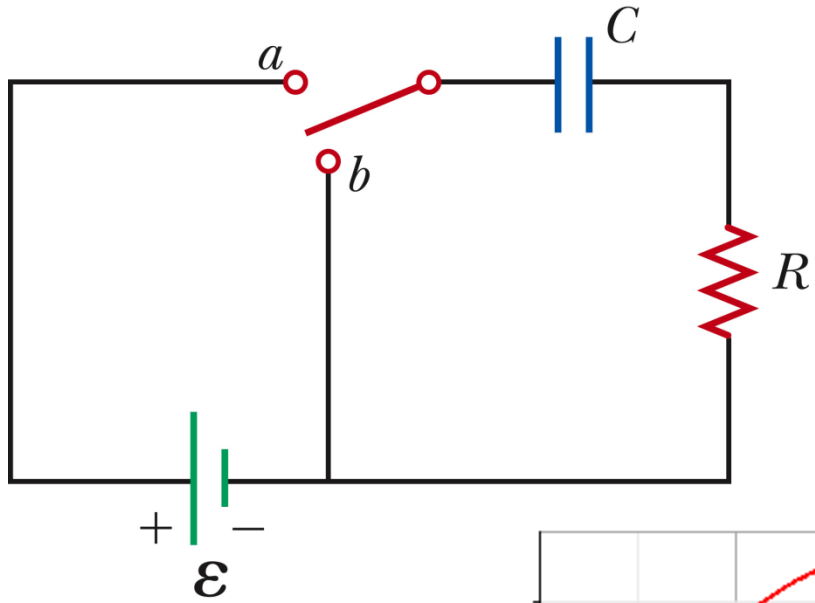


$$\frac{Q}{C\mathcal{E}}$$

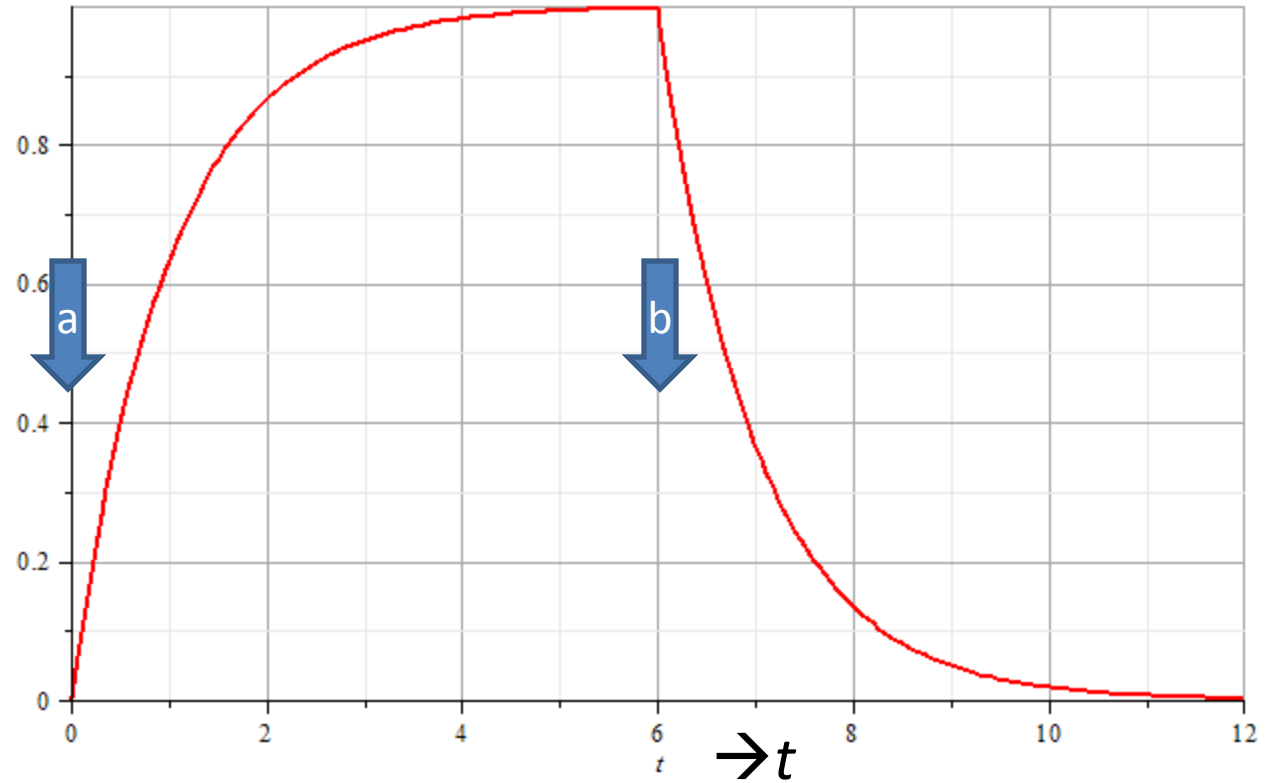

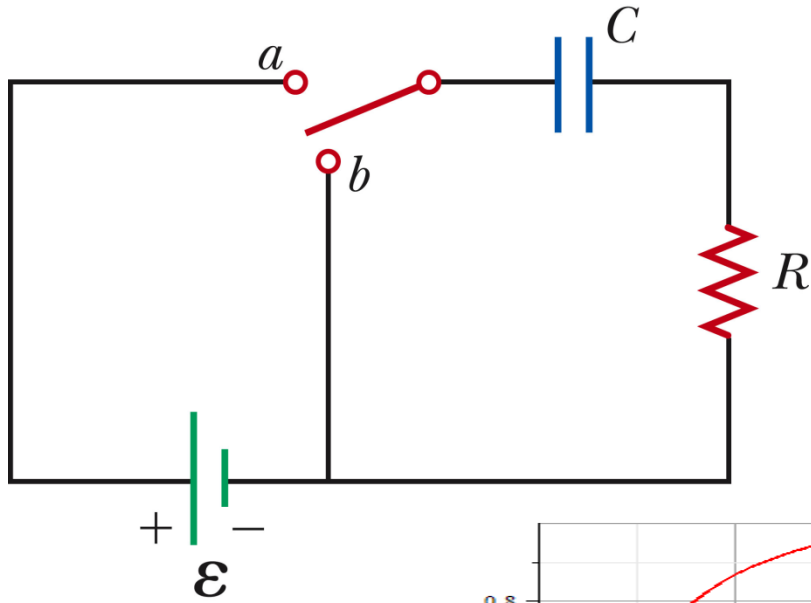


$$\frac{Q}{C\mathcal{E}}$$

$$\frac{I}{\mathcal{E}/R}$$

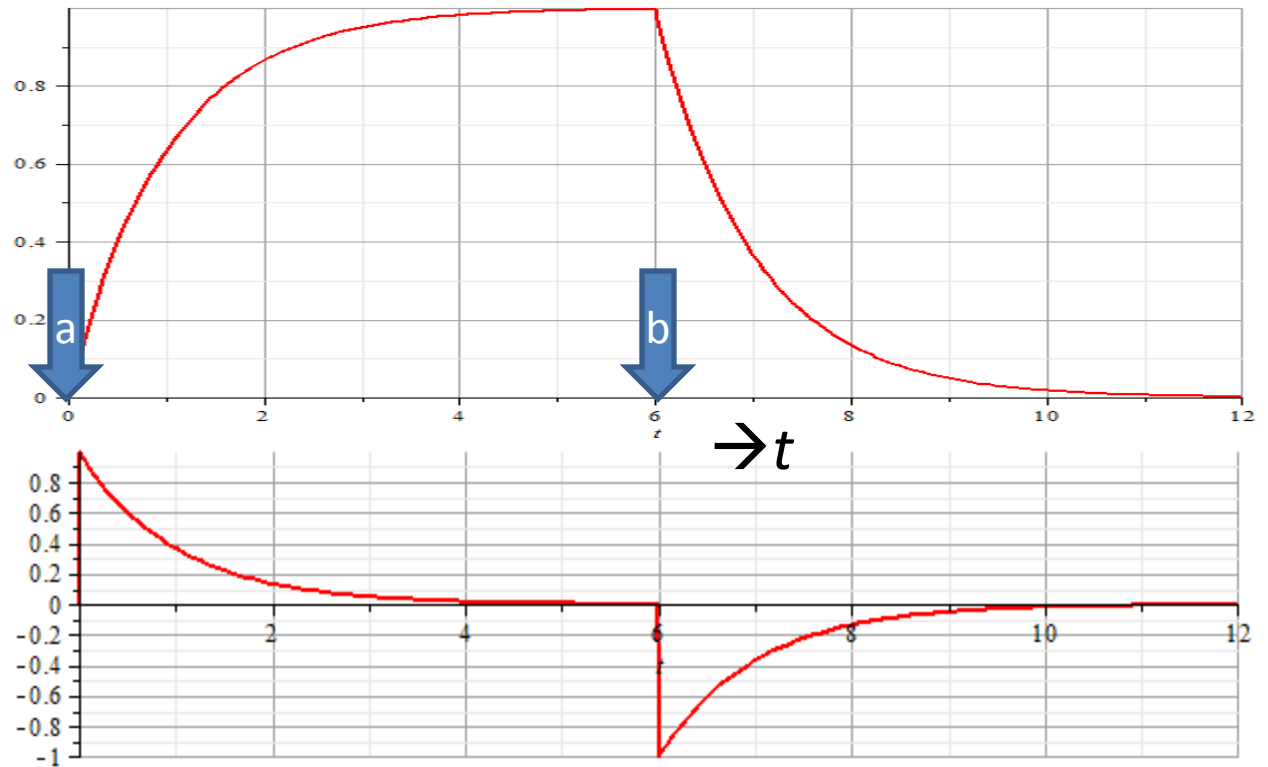

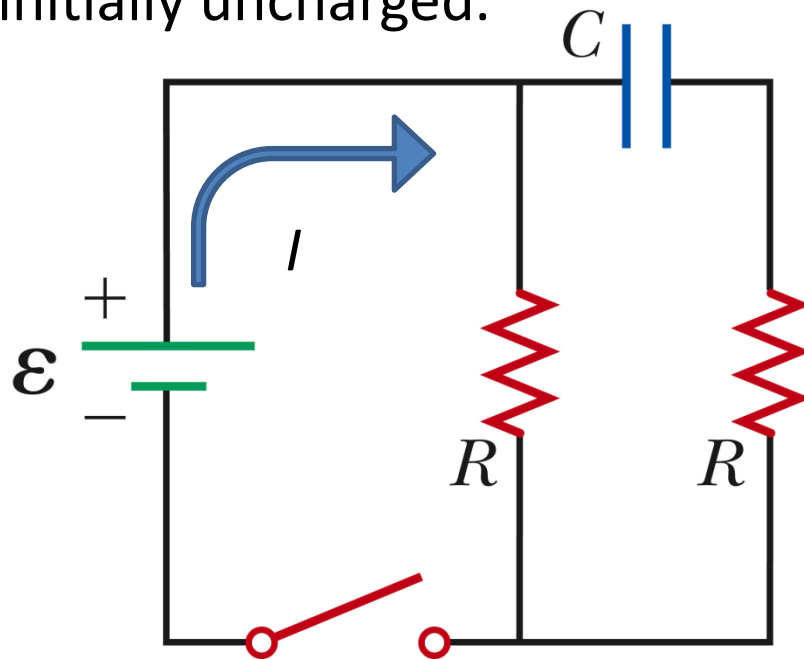Example 28.5 :

Assume the capacitor is initially uncharged.




What is the current I flowing through the battery just when the switch is closed?

- A. 0
- B. $\mathcal{E}/2R$
- C. \mathcal{E}/R
- D. $2\mathcal{E}/R$

What is the current I flowing through the battery after the switch has been closed for a long time?

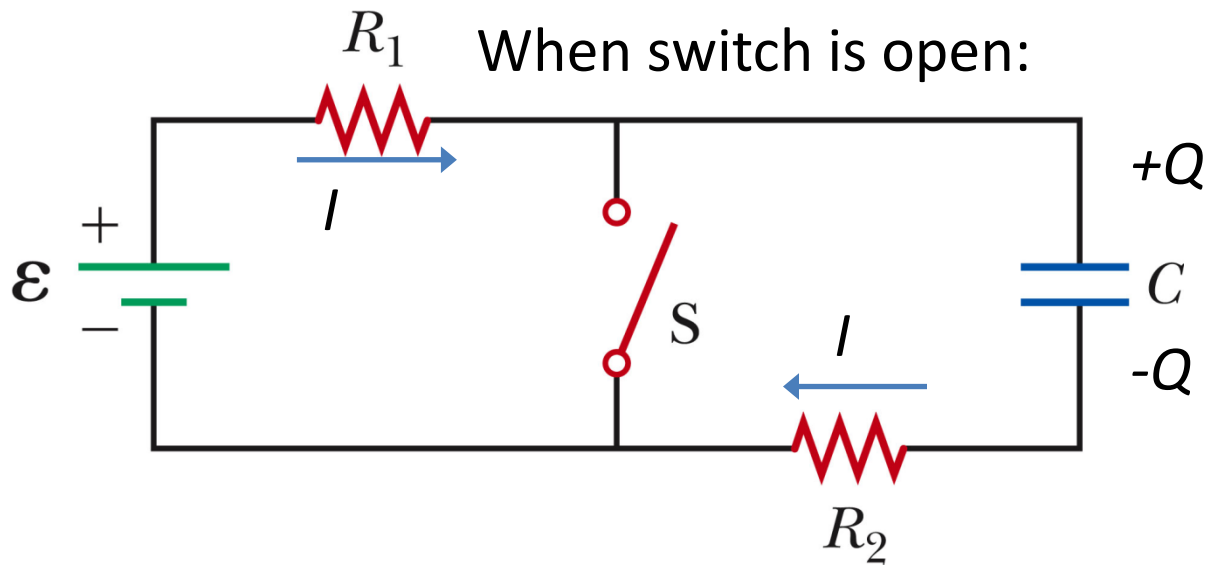- A. 0
- B. $\mathcal{E}/2R$
- C. \mathcal{E}/R
- D. $2\mathcal{E}/R$



$$\mathcal{E} - IR_1 - \frac{Q}{C} - IR_2 = 0$$

$$I(R_1 + R_2) = \mathcal{E} - \frac{Q}{C}$$

$$\frac{dQ}{dt}(R_1 + R_2) = \mathcal{E} - \frac{Q}{C}$$


$$\frac{dQ}{dt} = -\frac{1}{(R_1 + R_2)C}(Q - C\mathcal{E})$$

$$Q(t) = C\mathcal{E}(1 - e^{-t/\tau}) \quad \text{where } \tau \equiv (R_1 + R_2)C$$

$$\text{For } t \gg \tau: Q(t \rightarrow \infty) = C\mathcal{E}$$

$$I(t \rightarrow \infty) = \frac{C\mathcal{E}}{\tau} e^{-t/\tau} \Big|_{t \rightarrow \infty} = 0$$

When switch is closed (reset $t=0$):

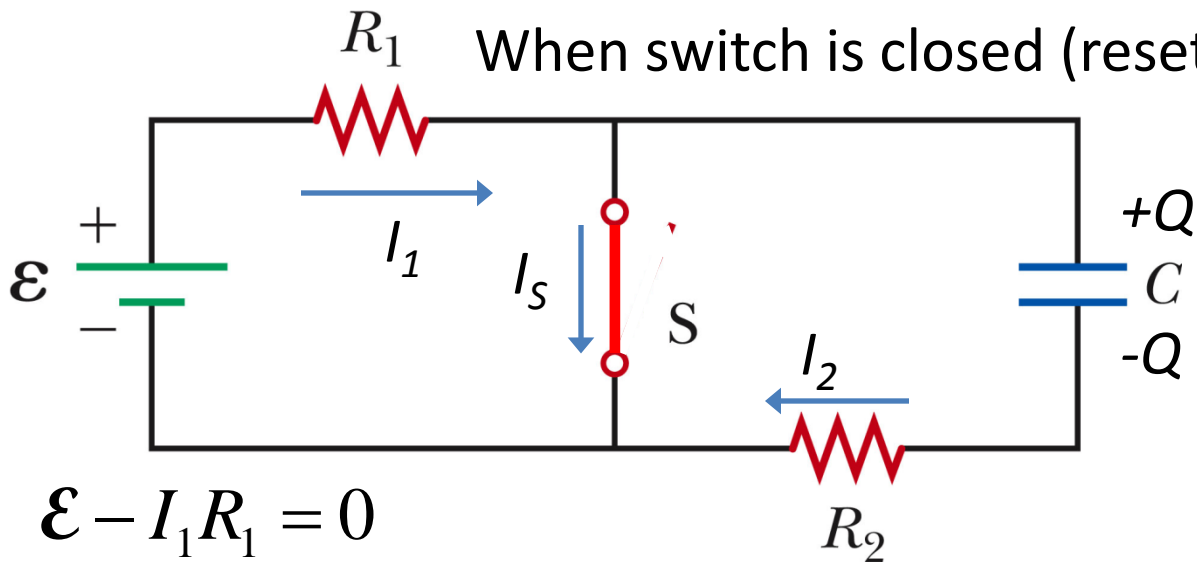

$$\mathcal{E} - I_1 R_1 = 0$$

$$-\frac{Q}{C} - I_2 R_2 = 0$$

$$I_2 = \frac{dQ}{dt} \Rightarrow Q(t) = Q_0 e^{-t/\tau}$$

$$\tau \equiv R_2 C \quad \text{and} \quad Q_0 \equiv C\mathcal{E}$$

$$I_2 = \frac{dQ}{dt} = -\frac{C\mathcal{E}}{\tau} e^{-t/\tau} = -\frac{\mathcal{E}}{R_2} e^{-t/\tau}$$

Current through switch :

$$I_1 = I_2 + I_S = 0$$

$$I_S = I_1 - I_2 = \frac{\mathcal{E}}{R_1} + \frac{\mathcal{E}}{R_2} e^{-t/\tau}$$