

PHY 114 A General Physics II
11 AM-12:15 PM TR Olin 101

Plan for Lecture 9 (Chapter 28):

- 1. Direct-current circuits continued**
- 2. Voltage, resistor, and capacitor circuits**

2/21/2012 PHY 114 A Spring 2012 -- Lecture 8 1

5	02/02/2012	Electric potential	25.5-25.8	(Review for exam)	
	02/07/2012	Exam			
6	02/09/2012	Capacitance and dielectrics	26.1-26.7	26.4, 26.13, 26.30	02/14/2012
7	02/14/2012	Current and resistance	27.1-27.6	27.3, 27.12, 27.29	02/16/2012
8	02/16/2012	Direct current circuits	28.1-28.2	28.3, 28.7, 28.19	02/21/2012
9	02/21/2012	Direct current circuits	28.3-28.5	28.23, 28.25, 28.34	02/23/2012
10	02/23/2012	Review	26.1-28.5	(Review for exam)	
	02/28/2012	Exam			
11	03/01/2012	Magnetic fields	29.1-29.8	29.5, 29.32, 29.47	03/06/2012
12	03/06/2012	Magnetic field sources	30.1-30.6		
13	03/08/2012	Faraday's law	31.1-31.5		
	03/13/2012	No class (Spring Break)			
	03/15/2012	No class (Spring Break)			
14	03/20/2012	Induction and AC circuits	32.1-32.6		

Remember to send in your chapter reading questions...

2/21/2012 PHY 114 A Spring 2012 -- Lecture 8 2

Professor George Holzwarth (gholz@wfu.edu) will administer the exam on 2/28/2012 and will lecture on magnetic fields, electric motors, etc. on 3/1/2012.

2/21/2012 PHY 114 A Spring 2012 -- Lecture 8 3

Circuit diagram:
 Example project from web page
<http://www.kpsec.freeuk.com/projects/dummy.htm>

2/21/2012 PHY 114 A Spring 2012 – Lecture 8 4

From webassign:
 Consider the circuit shown in the figure below. (Let $R_1 = 3.00 \Omega$, $R_2 = 4.00 \Omega$, and $\mathcal{E} = 6.00 \text{ V}$.)

(a) Find the voltage across R_1 .
 V

(b) Find the current in R_1 .
 A

$\mathcal{E} - 2I - R_1 I_1 = 0$
 $\Delta V_1 = R_1 I_1 = \mathcal{E} - 2I$
 among the many ways to find I :

$$I = \frac{\mathcal{E}}{R_{eq}}$$

2/21/2012 PHY 114 A Spring 2012 – Lecture 8 5


Circuits involving Voltage, Capacitance, and Resistance

Open switch
 → no charge or current

Switch closed
 → VCR circuit

Switch closed
 → RC circuit

2 114 A Spring 2012 – Lecture 8 6

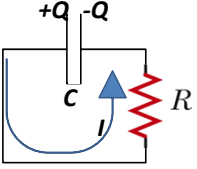

$$-\frac{Q}{C} - IR = 0$$

$$I = \frac{dQ}{dt}$$

$$-\frac{Q}{C} - \frac{dQ}{dt} R = 0$$

$$\frac{dQ}{dt} = -\frac{1}{RC} Q$$

2/21/2012 PHY 114 A Spring 2012 -- Lecture 8 7

What are the units of RC?

- A. Seconds
- B. Cycles per second
- C. Meters
- D. Coulombs
- E. Volts

2/21/2012 PHY 114 A Spring 2012 -- Lecture 8 8


Simple rate equation for growth :

$$\frac{dM}{dt} = rM \quad \frac{dM}{dt} = \text{rate of accumulation of money}$$

r = rate of increase
 $M = M(t)$ = money at time t

Analysis:

$$\frac{dM}{dt} = rM \Rightarrow \frac{dM}{M} = d \ln(M) = r dt$$
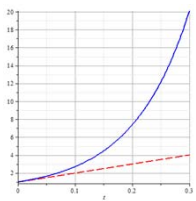
$$\ln(M) \Big|_{M_0}^M = r t \Big|_{t_0}^t \Rightarrow M(t) = M_0 e^{r(t-t_0)}$$


2/21/2012 PHY 114 A Spring 2012 -- Lecture 8 9

Simple rate equation for decrease :


$$\frac{dM}{dt} = -rM \quad \frac{dM}{dt} = \text{rate of accumulation of money}$$

$$r = \text{rate of decrease}$$


$$M = M(t) = \text{money at time } t$$

Analysis:


$$\frac{dM}{dt} = -rM \Rightarrow \frac{dM}{M} = d \ln(M) = -r dt$$
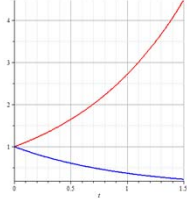
$$\ln(M) \Big|_{M_0}^M = -rt \Big|_{t_0}^t \Rightarrow M(t) = M_0 e^{-r(t-t_0)}$$

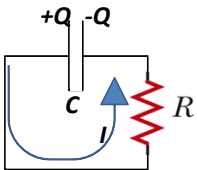
2/21/2012 PHY 114 A Spring 2012 -- Lecture 8 10




$$\frac{dQ}{dt} = -\frac{1}{RC} Q = -\frac{1}{\tau} Q$$
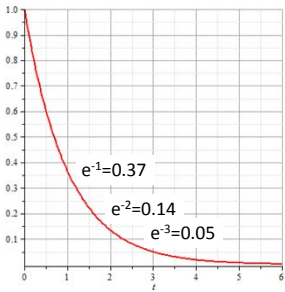
$$Q(t) = Q_0 e^{-(t-t_0)/\tau}$$


2/21/2012 PHY 114 A Spring 2012 -- Lecture 8 11

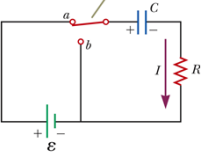Charging capacitor:
Switch closed at $t=0$; $Q(t=0)=0$




$$\varepsilon - \frac{Q}{C} - IR = 0 = \varepsilon - \frac{Q}{C} - \frac{dQ}{dt} R$$


$$\frac{dQ}{dt} = -\frac{1}{RC} (Q - C\varepsilon) \equiv -\frac{1}{\tau} (Q - C\varepsilon)$$

2/21/2012 PHY 114 A Spring 2012 -- Lecture 8 12

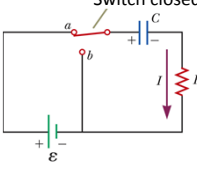Charging capacitor:
 Switch closed at $t=0$; $Q(t=0)=0$




$$\frac{dQ}{dt} = -\frac{1}{RC}(Q - C\mathcal{E}) \equiv -\frac{1}{\tau}(Q - C\mathcal{E})$$
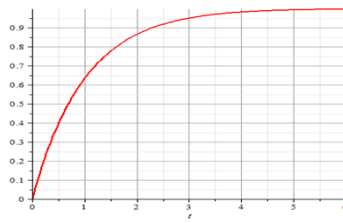
$$Q(t) = C\mathcal{E}(1 - e^{-t/\tau})$$


2/21/2012 PHY 114 A Spring 2012 – Lecture 8 13


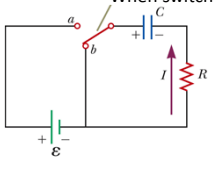
Discharging capacitor
 When switch closed $Q(t_c)=C\mathcal{E}$




$$\frac{dQ}{dt} = -\frac{1}{RC}Q = -\frac{1}{\tau}Q$$

$$Q(t) = C\mathcal{E}e^{-(t-t_c)/\tau}$$

2/21/2012 PHY 114 A Spring 2012 – Lecture 8 14

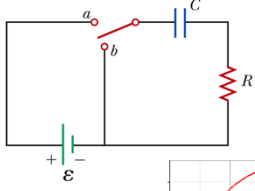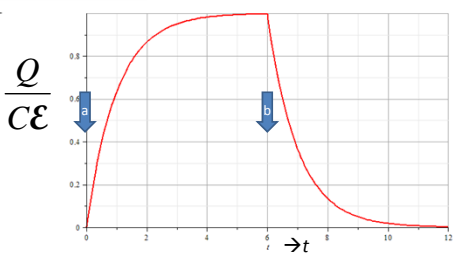2/21/2012 PHY 114 A Spring 2012 – Lecture 8 15

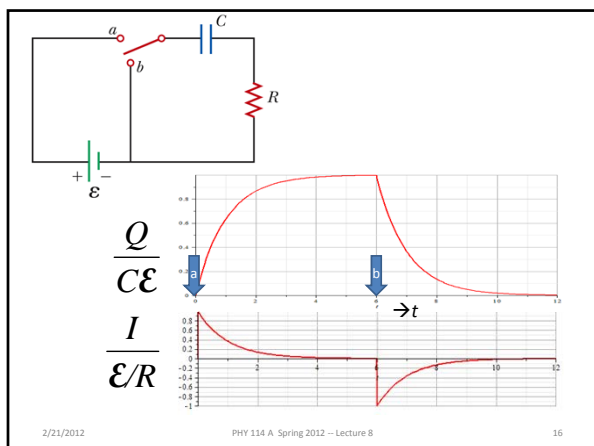

Example 28.5 :
Assume the capacitor is initially uncharged.

What is the current I flowing through the battery just when the switch is closed?

A. 0
B. $\mathcal{E}/2R$
C. \mathcal{E}/R
D. $2\mathcal{E}/R$

What is the current I flowing through the battery after the switch has been closed for a long time?

A. 0
B. $\mathcal{E}/2R$
C. \mathcal{E}/R
D. $2\mathcal{E}/R$

2/21/2012 PHY 114 A Spring 2012 – Lecture 8 17

When switch is open:

$$\mathcal{E} - IR_1 - \frac{Q}{C} - IR_2 = 0$$

$$I(R_1 + R_2) = \mathcal{E} - \frac{Q}{C}$$

$$\frac{dQ}{dt}(R_1 + R_2) = \mathcal{E} - \frac{Q}{C}$$

$$\frac{dQ}{dt} = -\frac{1}{(R_1 + R_2)C}(Q - C\mathcal{E})$$


$$Q(t) = C\mathcal{E}(1 - e^{-t/\tau}) \quad \text{where } \tau \equiv (R_1 + R_2)C$$

For $t \gg \tau$: $Q(t \rightarrow \infty) = C\mathcal{E}$

$$I(t \rightarrow \infty) = \frac{C\mathcal{E}}{\tau} e^{-t/\tau} \Big|_{t \rightarrow \infty} = 0$$

2/21/2012 PHY 114 A Spring 2012 – Lecture 8 18

When switch is closed (reset $t=0$):

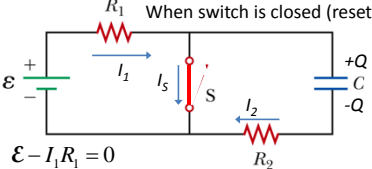

$\mathcal{E} - I_1 R_1 = 0$
 $-\frac{Q}{C} - I_2 R_2 = 0$
 $I_2 = \frac{dQ}{dt} \Rightarrow Q(t) = Q_0 e^{-t/\tau}$
 $\tau \equiv R_2 C$ and $Q_0 \equiv C\mathcal{E}$
 $I_2 = \frac{dQ}{dt} = -\frac{C\mathcal{E}}{\tau} e^{-t/\tau} = -\frac{\mathcal{E}}{R_2} e^{-t/\tau}$

Current through switch:

$I_1 = I_2 + I_S = 0$
 $I_S = I_1 - I_2 = \frac{\mathcal{E}}{R_1} + \frac{\mathcal{E}}{R_2} e^{-t/\tau}$

2/21/2012 PHY 114 A Spring 2012 -- Lecture 8 19
