


Alternating Current (AC) Circuits

- AC Voltages and Phasors
- Resistors, Inductors and Capacitors in AC Circuits
- RLC Circuits
- Power and Resonance
- Transformers

AC Sources

- AC sources have voltages and currents that vary sinusoidally.
- The current in a circuit driven by an AC source also oscillates at the same frequency.
- The standard AC frequency in the US is 60 Hz (337 rad/s).
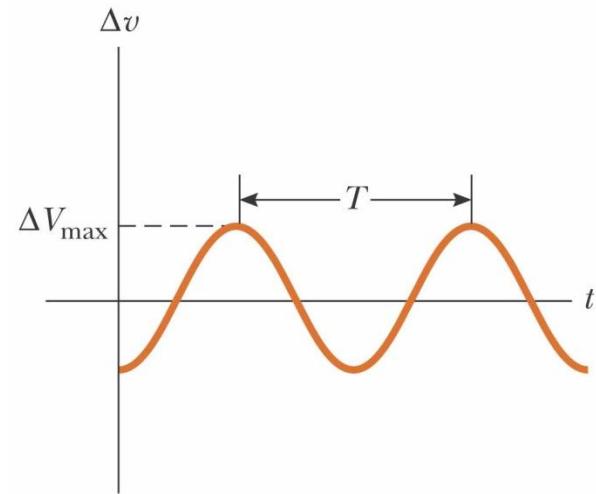
$$\Delta v(t) = \Delta V_{\max} \sin(\omega t)$$





©2004 Thomson - Brooks/Cole

$$T = \frac{1}{f} = \frac{2\pi}{\omega}$$


Phasors

Consider a sinusoidal voltage source: $\Delta v(t) = \Delta V_{\max} \sin(\omega t)$

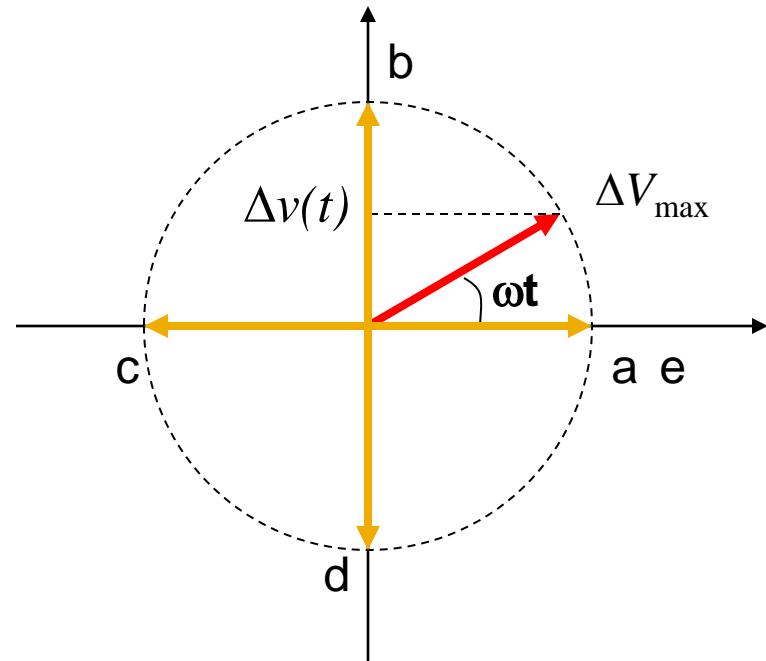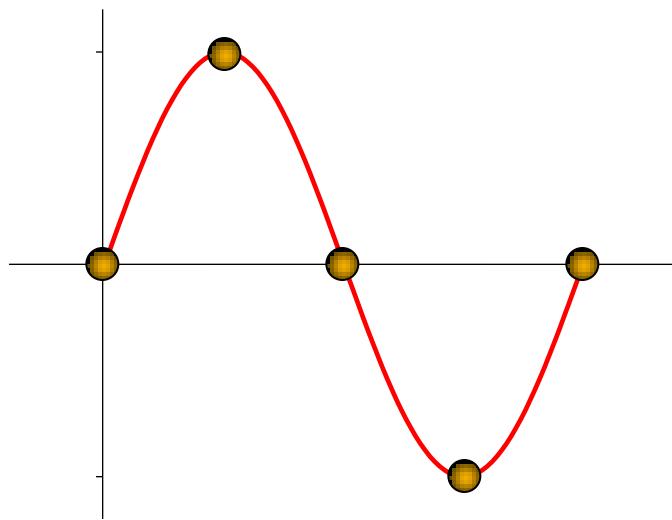This source can be represented graphically as a vector called a **phasor**:




Resistors in AC Circuits

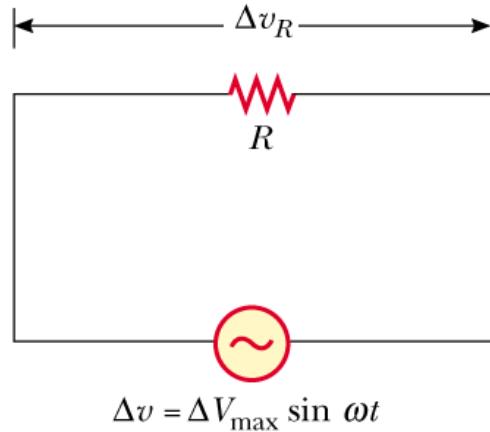


$$\Delta v - \Delta v_R = 0$$
$$\Delta V_{\max} \sin \omega t = \Delta v_R$$

$$i_R = \frac{\Delta v_R}{R} = \frac{\Delta V_{\max}}{R} \sin \omega t = I_{\max} \sin \omega t$$
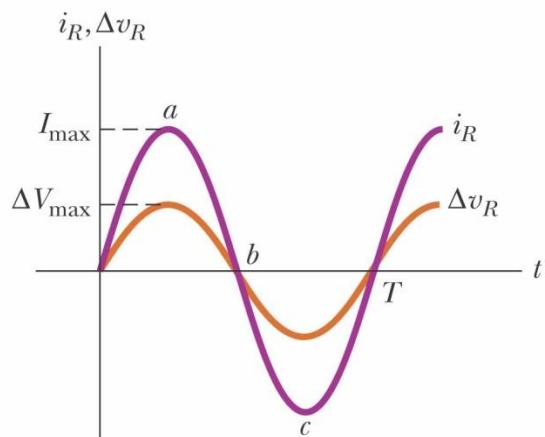
$$I_{\max} = \frac{\Delta V_{\max}}{R}$$
$$\Delta v_R = I_{\max} R \sin \omega t$$



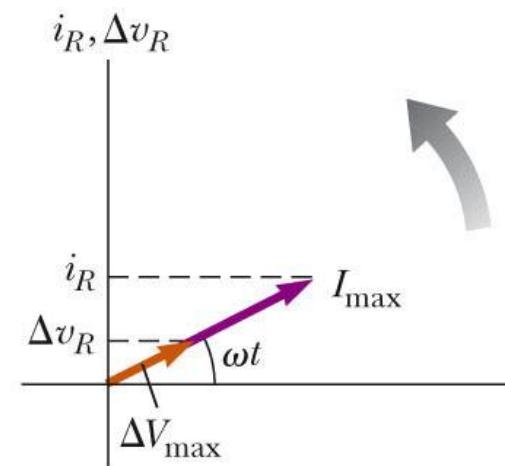Since both have the same arguments in the sine term, i_R and Δv_R are in line, they are **in phase**.



Root Mean Square (RMS) Current and Voltage


$$i_R = I_{\max} \sin \omega t$$

$$\mathcal{P}(t) = R i_R^2 = R I_{\max}^2 \sin^2 \omega t$$


$$\mathcal{P}(t) = R i_R^2 = R I_{\max}^2 \sin^2 \omega t$$

$$\mathcal{P}_{av} = R I_{\max}^2 \left(\frac{1}{2} \right) = I_{rms}^2 R$$
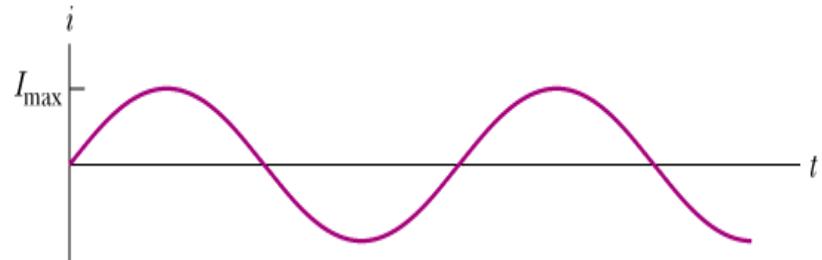
$$I_{rms} = \frac{I_{\max}}{\sqrt{2}} = 0.707 I_{\max}$$




(a)

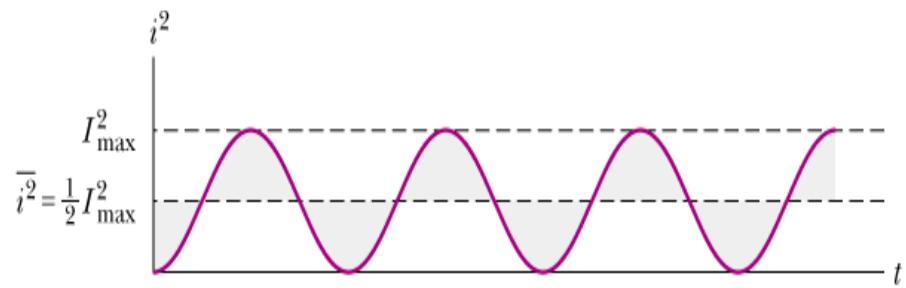


(b)

$$\Delta V_{rms} = \frac{\Delta V_{\max}}{\sqrt{2}} = 0.707 \Delta V_{\max}$$

Inductors in AC Circuits

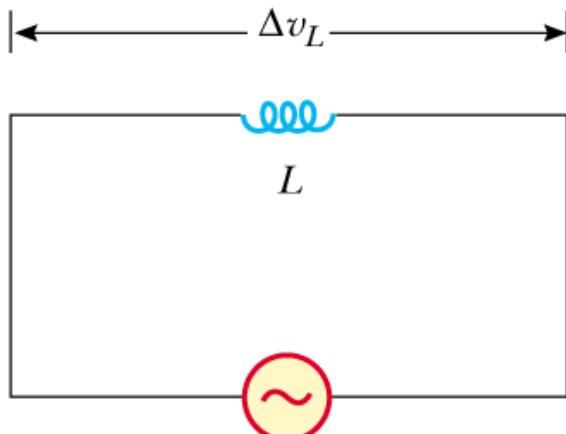
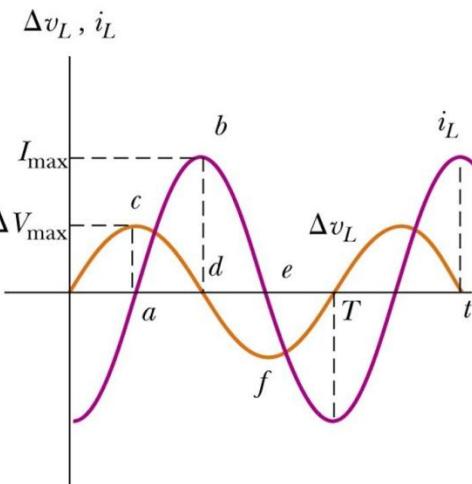
$$\Delta v = \Delta V_{\max} \sin \omega t$$



$$\Delta v - \Delta v_L = 0$$

$$\Delta V_{\max} \sin \omega t = L \frac{di}{dt}$$

$$di = \frac{\Delta V_{\max}}{L} \sin \omega t dt$$

$$i_L = \int di = -\frac{\Delta V_{\max}}{\omega L} \cos \omega t$$


$$i_L = \frac{\Delta V_{\max}}{\omega L} \sin \left(\omega t - \frac{\pi}{2} \right)$$

$$I_{\max} = \frac{\Delta V_{\max}}{\omega L} = \frac{\Delta V_{\max}}{X_L}$$


Inductive Reactance

$$\Delta v_L = -I_{\max} X_L \sin \omega t$$

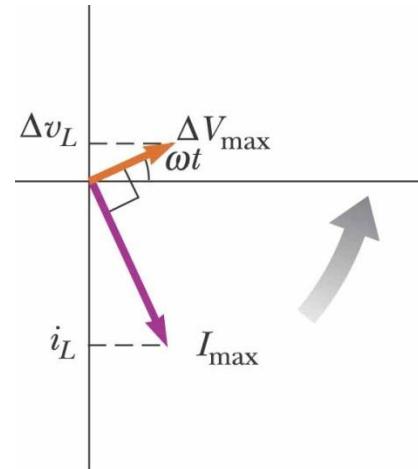For a sinusoidal voltage, the current in the inductor always **lags** the voltage across it by 90° .



Capacitors in AC Circuits

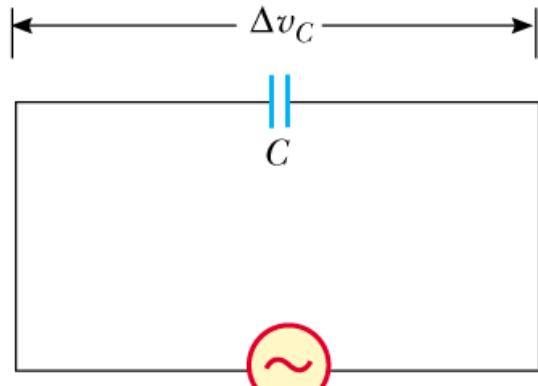


$$\Delta v = \Delta V_{\max} \sin \omega t$$

$$\Delta v = \Delta v_C = \Delta V_{\max} \sin \omega t$$

$$q = C \Delta V_{\max} \sin \omega t$$

$$i_C = \frac{dq}{dt} = \omega C \Delta V_{\max} \cos \omega t$$
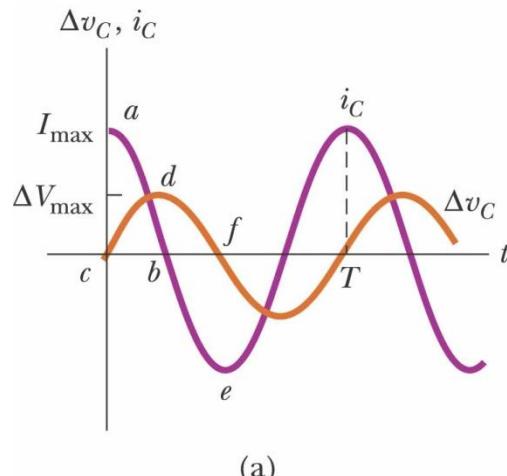
$$i_C = \omega C \Delta V_{\max} \sin\left(\omega t + \frac{\pi}{2}\right)$$




For a sinusoidal voltage, the current in the capacitor always **leads** the voltage across it by 90° .

$$I_{\max} = \omega C \Delta V_{\max} = \frac{\Delta V_{\max}}{X_C}$$



$$X_C = \frac{1}{\omega C}$$

Capacitive Reactance
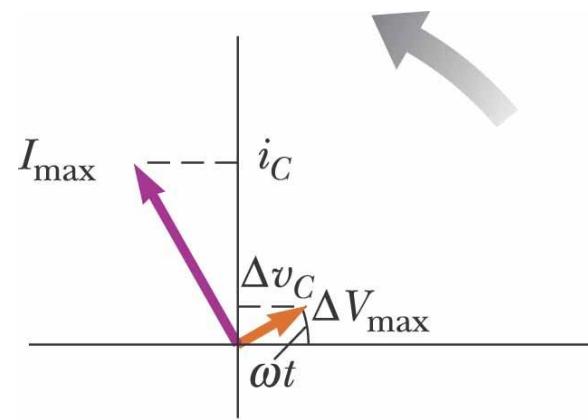
$$\Delta v_C = I_{\max} X_C \sin \omega t$$



RLC Series Circuit

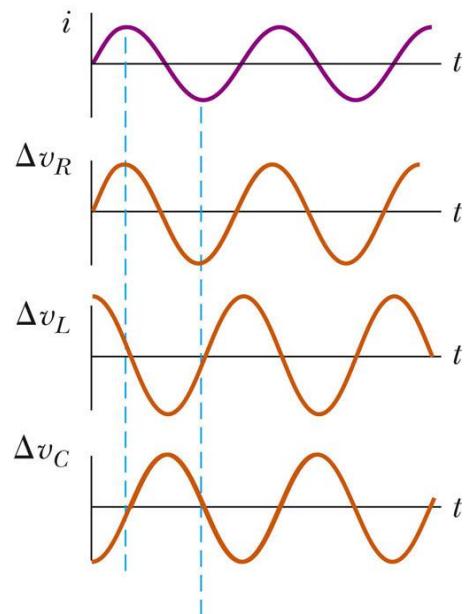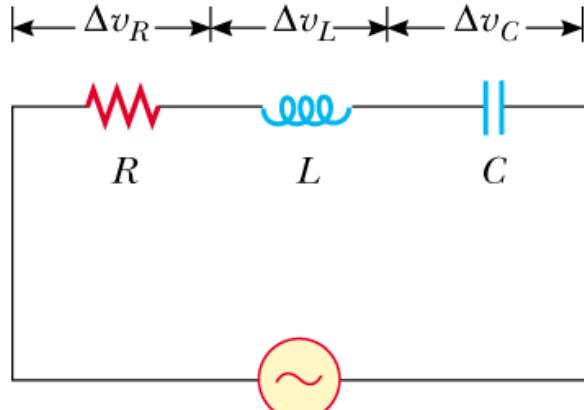

$$\Delta v = \Delta V_{\max} \sin \omega t$$

$$i = I_{\max} \sin(\omega t - \phi)$$



$$\Delta v_R = I_{\max} R \sin \omega t = \Delta V_R \sin \omega t$$

$$\Delta v_L = I_{\max} X_L \sin\left(\omega t + \frac{\pi}{2}\right) = \Delta V_L \cos \omega t$$

$$\Delta v_C = I_{\max} X_C \sin\left(\omega t - \frac{\pi}{2}\right) = -\Delta V_C \cos \omega t$$

$$\Delta v = \Delta v_R + \Delta v_L + \Delta v_C$$

Using Phasors in a RLC Circuit

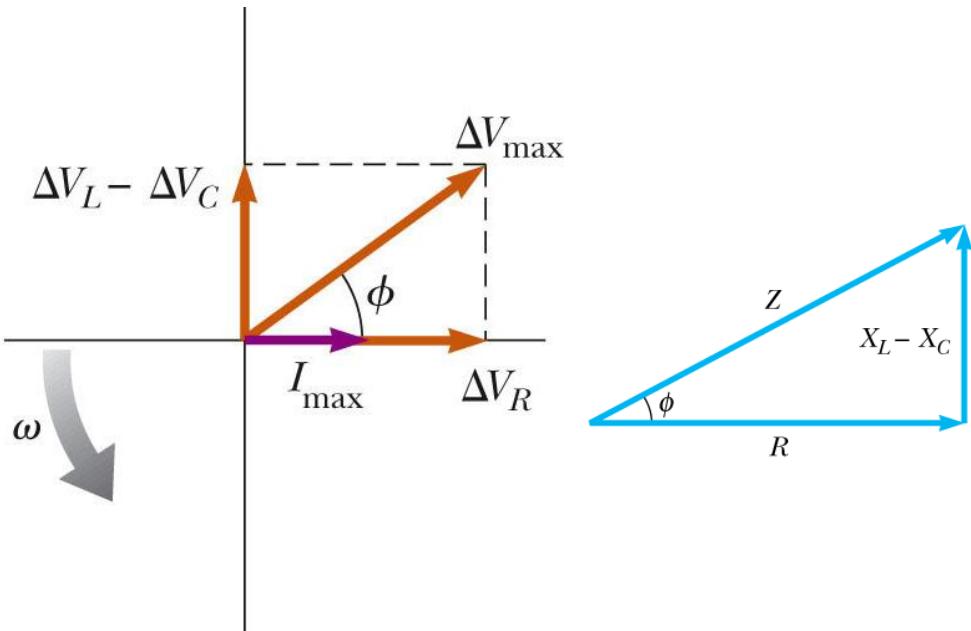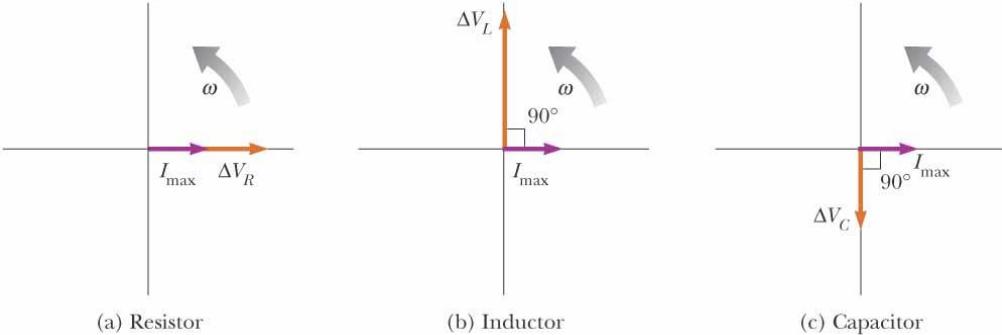

$$\Delta V_{\max} = \sqrt{\Delta V_R^2 + (\Delta V_L - \Delta V_C)^2}$$

$$\Delta V_{\max} = \sqrt{(I_{\max} R)^2 + (I_{\max} X_L - I_{\max} X_C)^2}$$

$$\Delta V_{\max} = I_{\max} \sqrt{R^2 + (X_L - X_C)^2}$$

$$I_{\max} = \frac{\Delta V_{\max}}{\sqrt{R^2 + (X_L - X_C)^2}}$$


$$Z \equiv \sqrt{R^2 + (X_L - X_C)^2}$$

Impedance

$$\Delta V_{\max} = I_{\max} Z$$

$$\phi = \tan^{-1} \left(\frac{X_L - X_C}{R} \right)$$

Example 33.4

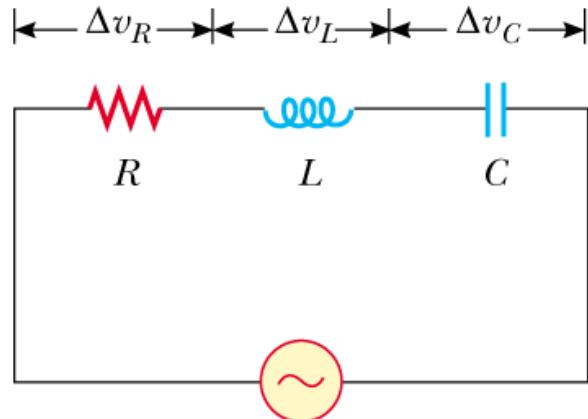

$$R = 425 \Omega$$

$$L = 1.25 \text{ H}$$

$$C = 3.5 \mu\text{F}$$

$$\omega = 377 \text{ s}^{-1}$$

$$\Delta V_{\max} = 150 \text{ V}$$

$$X_L = \omega L = (377 \text{ s}^{-1})(1.25 \text{ H}) = 471 \Omega$$

$$X_C = \frac{1}{\omega C} = \frac{1}{(377 \text{ s}^{-1})(3.5 \mu\text{F})} = 758 \Omega$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2} = \sqrt{(425 \Omega)^2 + (471 \Omega - 758 \Omega)^2} = 513 \Omega$$

$$I_{\max} = \frac{\Delta V_{\max}}{Z} = \frac{150 \text{ V}}{513 \Omega} = 0.292 \text{ A}$$

$$\phi = \tan^{-1} \left(\frac{X_L - X_C}{R} \right) = \tan^{-1} \left(\frac{471 \Omega - 758 \Omega}{425 \Omega} \right) = -34^\circ$$

$$\Delta V_R = I_{\max} R = (0.292 \text{ A})(425 \Omega) = 124 \text{ V}$$

$$\Delta V_L = I_{\max} X_L = (0.292 \text{ A})(471 \Omega) = 138 \text{ V}$$

$$\Delta V_C = I_{\max} X_C = (0.292 \text{ A})(758 \Omega) = 221 \text{ V}$$

$$\Delta v_R = (124 \text{ V}) \sin 377t$$

$$\Delta v_L = (138 \text{ V}) \cos 377t$$

$$\Delta v_C = -(221 \text{ V}) \cos 377t$$

Power in an AC Circuit

$$\mathcal{P} = i\Delta v = I_{\max} \sin(\omega t - \phi) \Delta V_{\max} \sin \omega t$$

$$\mathcal{P} = I_{\max} \Delta V_{\max} (\sin \omega t \cos \phi - \cos \omega t \sin \phi) \sin \omega t$$

$$\mathcal{P} = I_{\max} \Delta V_{\max} \sin^2 \omega t \cos \phi - I_{\max} \Delta V_{\max} \sin \omega t \cos \omega t \sin \phi$$

$$\mathcal{P}_{av} = \frac{1}{2} I_{\max} \Delta V_{\max} \cos \phi$$

$$\mathcal{P}_{av} = I_{rms} \Delta V_{rms} \cos \phi$$

$$\Delta v_R = \Delta V_{\max} \cos \phi = I_{\max} R$$

$$\mathcal{P}_{av} = I_{rms} \left(\frac{\Delta V_{\max}}{\sqrt{2}} \right) \frac{I_{\max} R}{\Delta V_{\max}} = I_{rms} \frac{I_{\max} R}{\sqrt{2}}$$

$$\mathcal{P}_{av} = I_{rms}^2 R$$

No power loss occurs in an ideal capacitor or inductor.

For a purely resistive load, $\phi=0$

$$\mathcal{P}_{av} = I_{rms} \Delta V_{rms}$$

Resonance in Series RLC Circuits

A circuit is in resonance when its current is maximum.

$$I_{rms} = \frac{\Delta V_{rms}}{Z}$$

$$I_{rms} = \frac{\Delta V_{rms}}{\sqrt{R^2 + (X_L - X_C)^2}}$$

$I_{rms} = \text{max}$ when $X_L - X_C = 0$

$$X_L = X_C$$

$$\omega_0 L = \frac{1}{\omega_0 C}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

Resonance Frequency

Power in Series RLC Circuits


$$\mathcal{P}_{av} = I_{rms}^2 R = \frac{(\Delta V_{rms})^2}{Z^2} R = \frac{(\Delta V_{rms})^2 R}{R^2 + (X_L - X_C)^2}$$

$$(X_L - X_C)^2 = \left(\omega L - \frac{1}{\omega C} \right)^2 = \frac{L^2}{\omega^2} (\omega^2 - \omega_0^2)^2$$



$$\mathcal{P}_{av} = \frac{(\Delta V_{rms})^2 R \omega^2}{R^2 \omega^2 + L^2 (\omega^2 - \omega_0^2)^2}$$

$$\mathcal{P}_{av,\max} = \frac{(\Delta V_{rms})^2}{R} \quad \omega = \omega_0$$
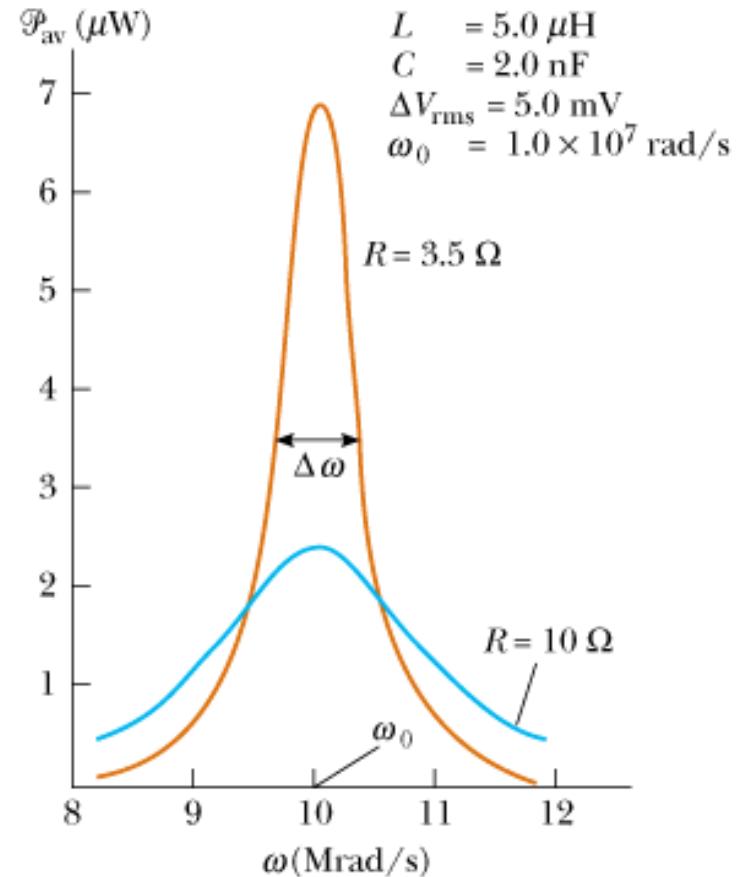
$$Q = \frac{\omega_0}{\Delta\omega} = \frac{\omega_0 L}{R} \quad \text{Quality Factor}$$



Transformers

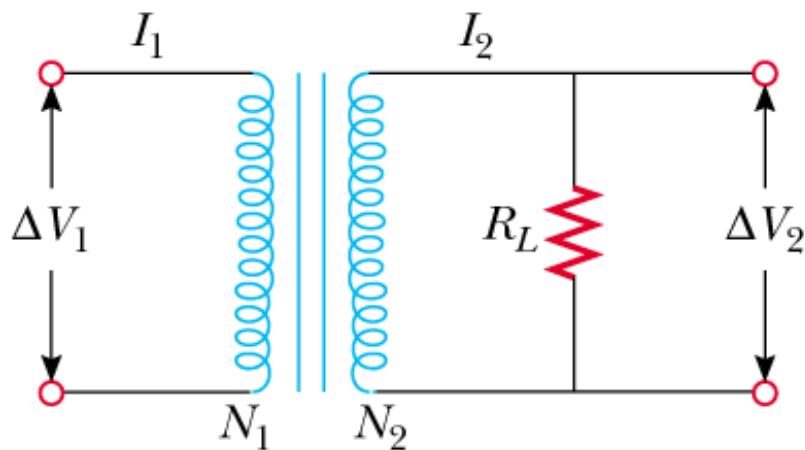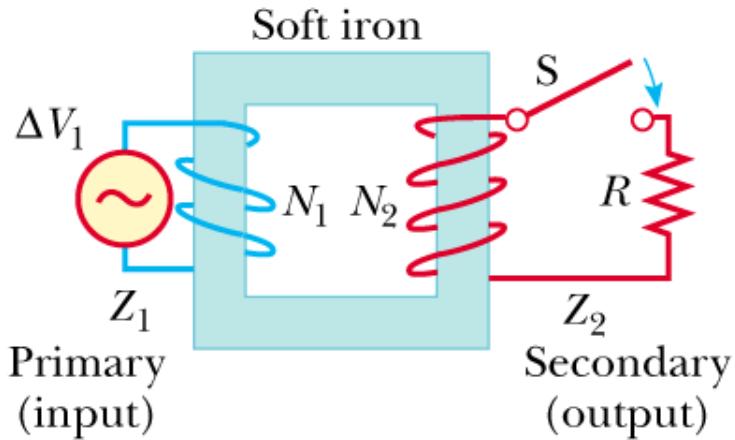

$$\Delta V_1 = -N_1 \frac{d\Phi_B}{dt}$$

$$\Delta V_2 = -N_2 \frac{d\Phi_B}{dt}$$

$$\Delta V_2 = \frac{N_2}{N_1} \Delta V_1$$

$$I_1 \Delta V_1 = I_2 \Delta V_2$$


$$I_2 = \frac{\Delta V_2}{R_L}$$

$$I_1 = \frac{\Delta V_1}{R_{eq}}$$


$$R_{eq} = \left(\frac{N_1}{N_2} \right)^2 R_L$$

Power Transmission

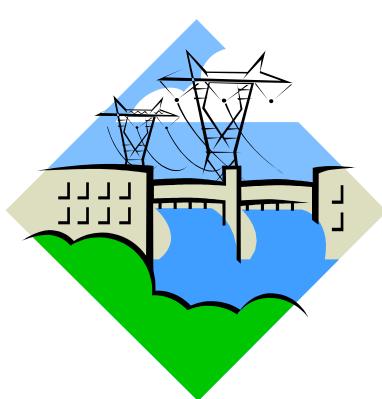
Power is transmitted in high voltage over long distances and then gradually stepped down to 240V by the time it gets to a house.



22 kV

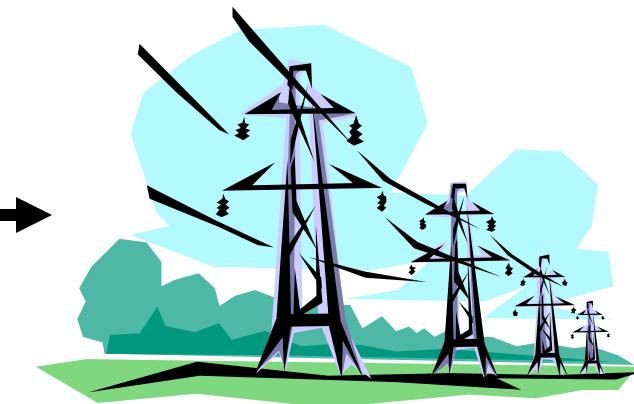

230 kV

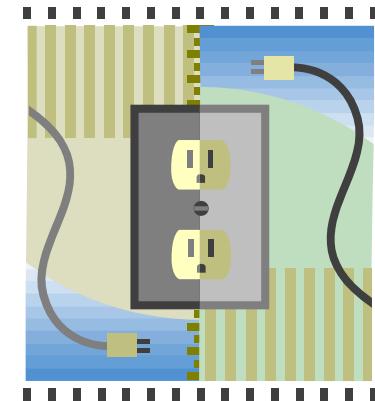

240 V

$$\mathcal{P}_g = 20 \text{ MW}$$

$$\text{Cost} = 10\text{¢/kWh}$$

$$I = \frac{\mathcal{P}_g}{\Delta V} = \frac{20 \times 10^6 \text{ W}}{230 \times 10^3 \text{ V}} = 87 \text{ A}$$

$$\mathcal{P} = I^2 R = (87 \text{ A})^2 (2 \Omega) = 15 \text{ kW}$$

$$\text{Total Cost} = (15 \text{ kW})(24 \text{ h})(\$0.1) = \$36$$

For 22kV transmission:

Total Cost = \$4100

For Next Class

- Midterm 2 Review on Tuesday
- Midterm 2 on Wednesday
- Reading Assignment for Thursday
 - Chapter 34 – Electromagnetic Waves
- WebAssign: Assignment 11 (due Tuesday, 5 PM)